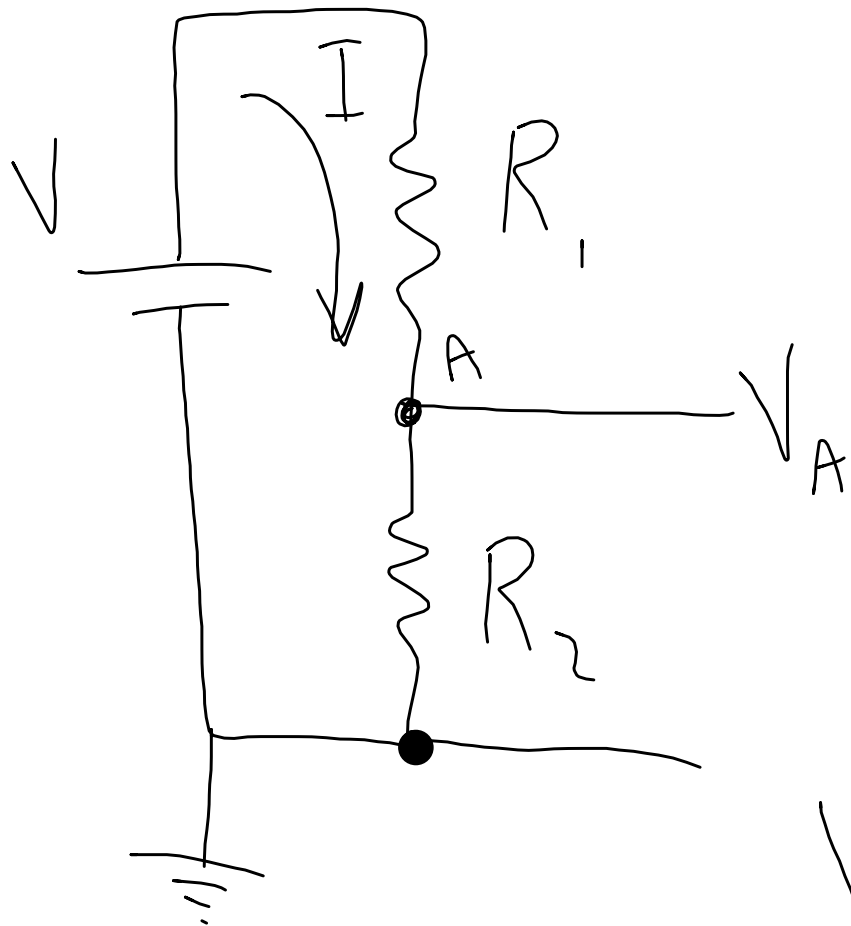


Voltage Divider





$$R_{eq} = R_1 + R_2$$

$$I = \frac{V}{R_1 + R_2}$$

$$V_A - 0 = I R_2$$

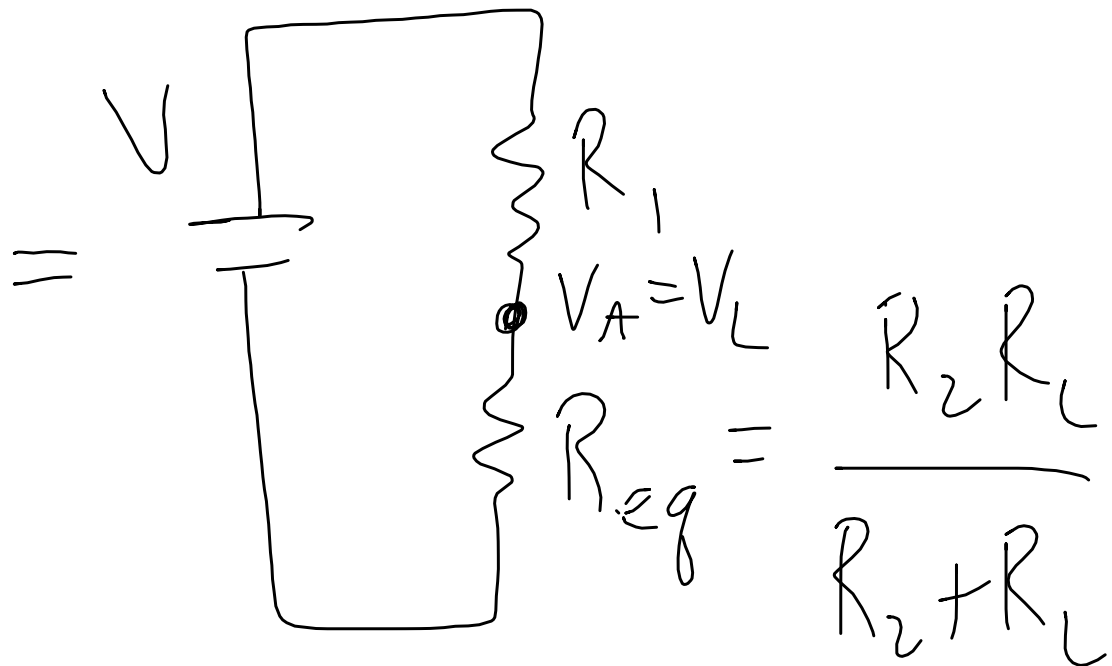
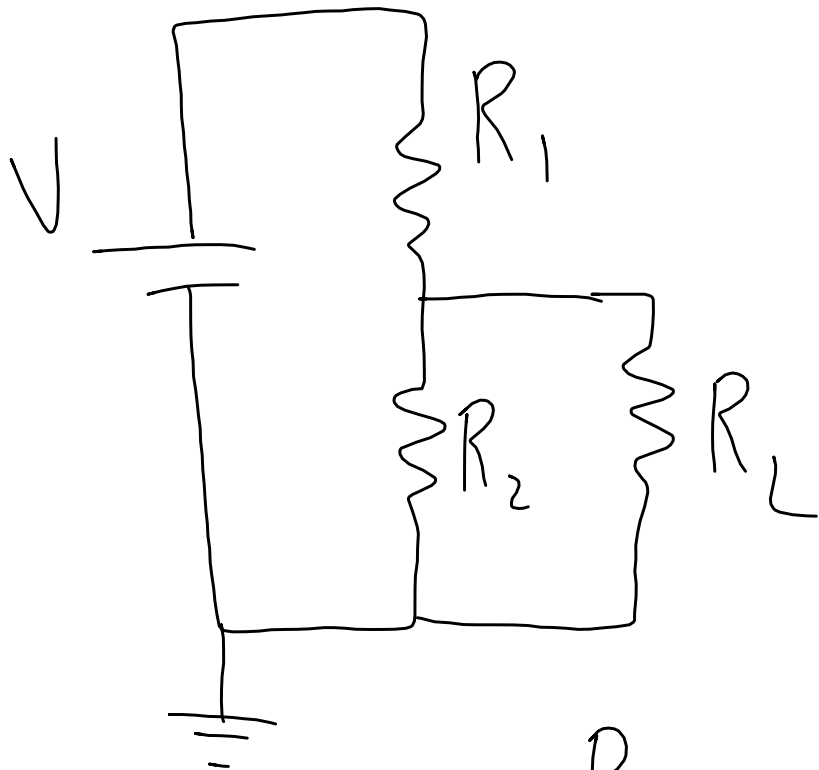
$$V_A = \frac{V}{R_1 + R_2} R_2 = V \left[\frac{R_2}{R_1 + R_2} \right]$$





$$V_L = V \frac{R_{eq}}{R_1 + R_{eq}} = \frac{R_2 R_L / (R_2 + R_L)}{R_1 + \frac{R_2 R_L}{R_2 + R_L}}$$

$$P_L = \frac{V_L^2}{R_L} \Rightarrow \text{Mathematica}$$

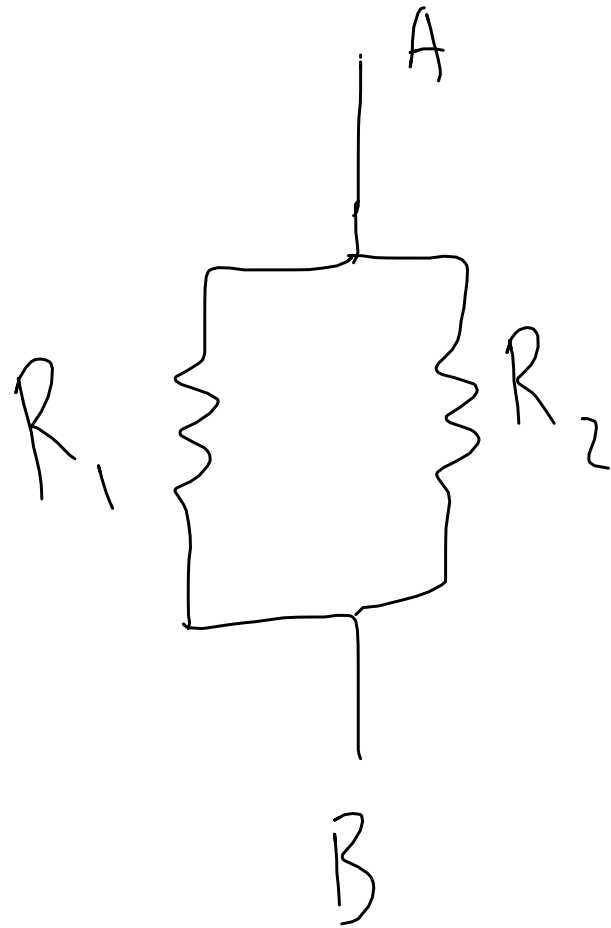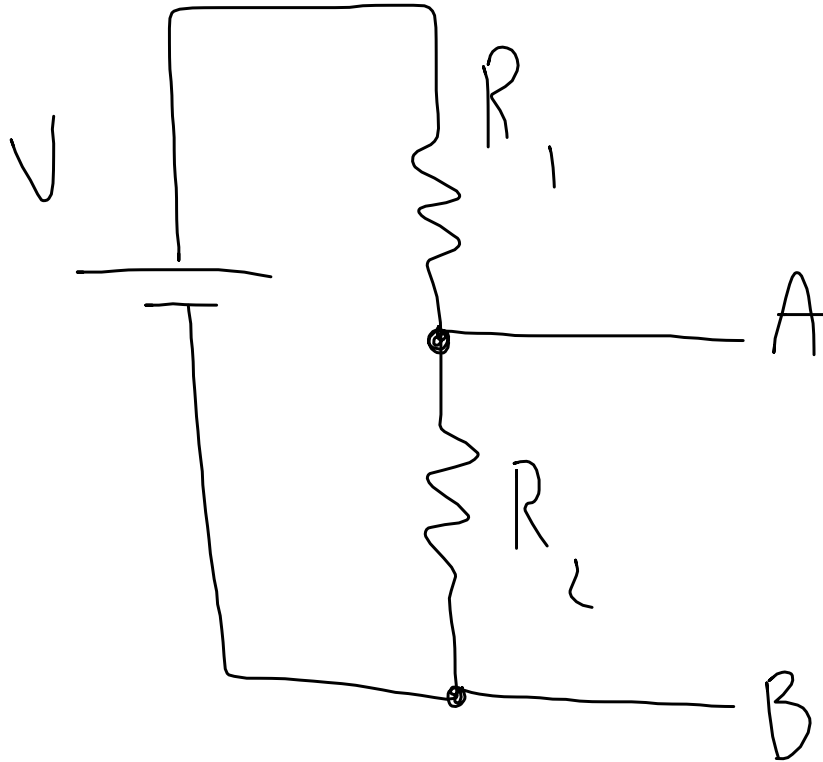Take $\frac{dP_L}{dR_L} = 0 \implies R_L = \frac{R_1 R_2}{R_1 + R_2}$



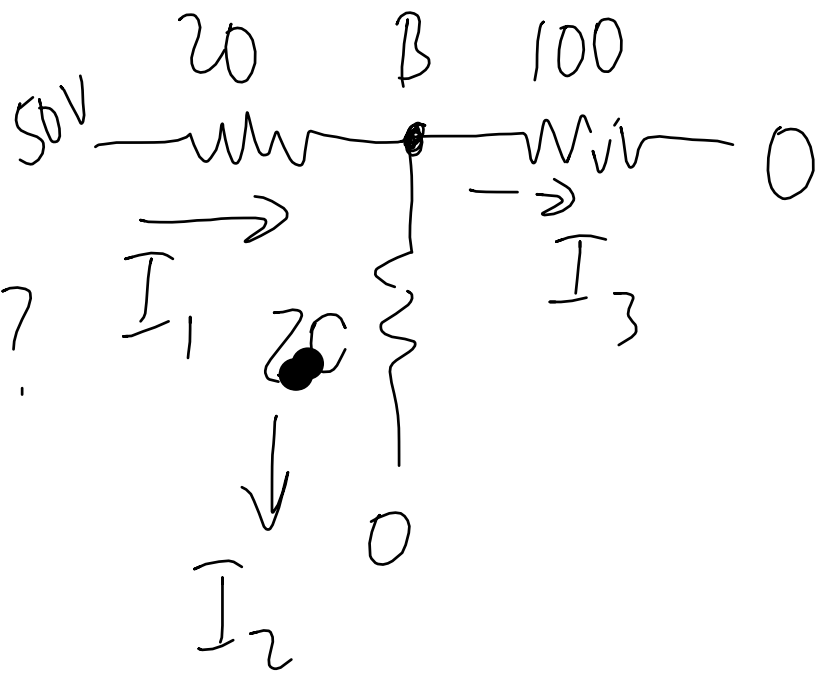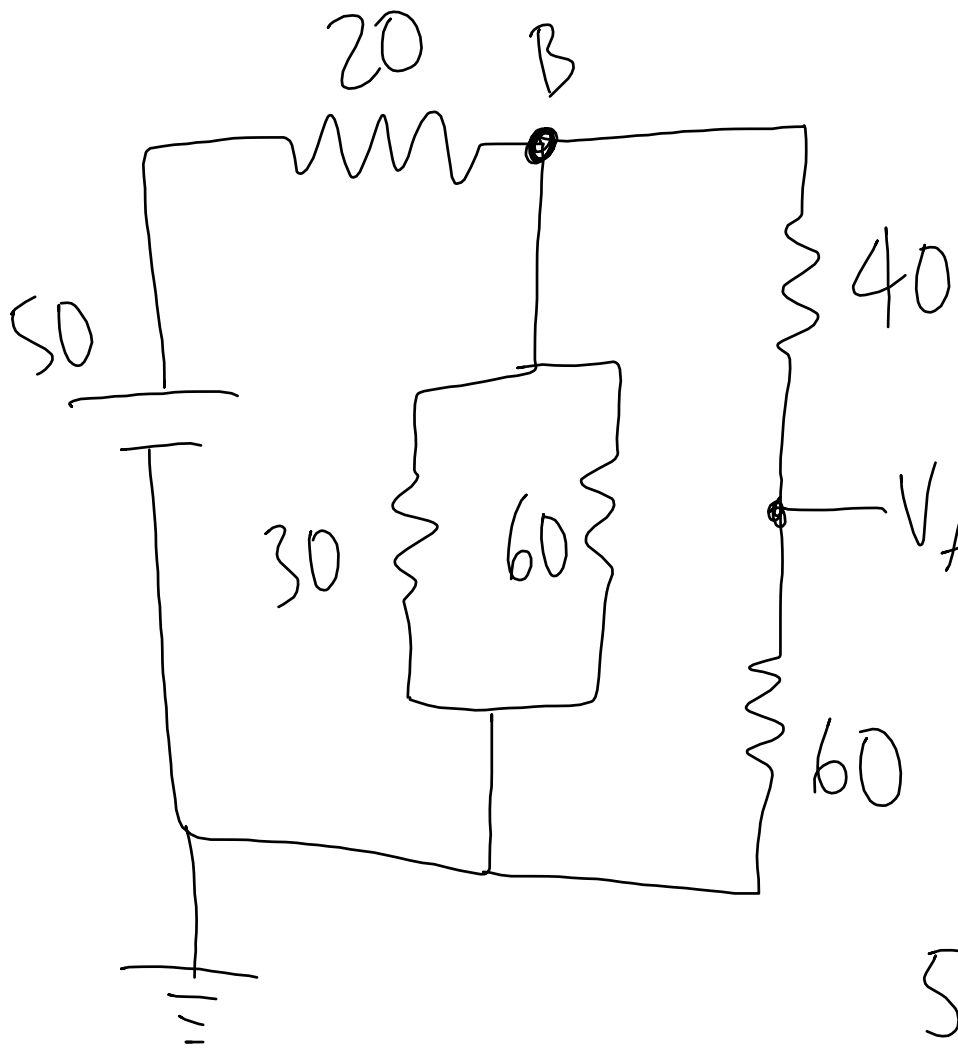

$$\frac{1}{R_{eq}} = \frac{1}{30} + \frac{1}{60} = \frac{3}{60}$$

$$50 - V_B = I_1 \cdot 20$$

$$V_B = I_2 \cdot 20$$

$$V_B = I_3 \cdot 100$$


$$I_1 = I_2 + I_3$$

Math: $V_B = 22.73$

$$V_A = 0.6 V_B = 13.64 \text{ V}$$



Attach load R_L between A & ground,
 ↓ everything changes!

Thevenin's theorem

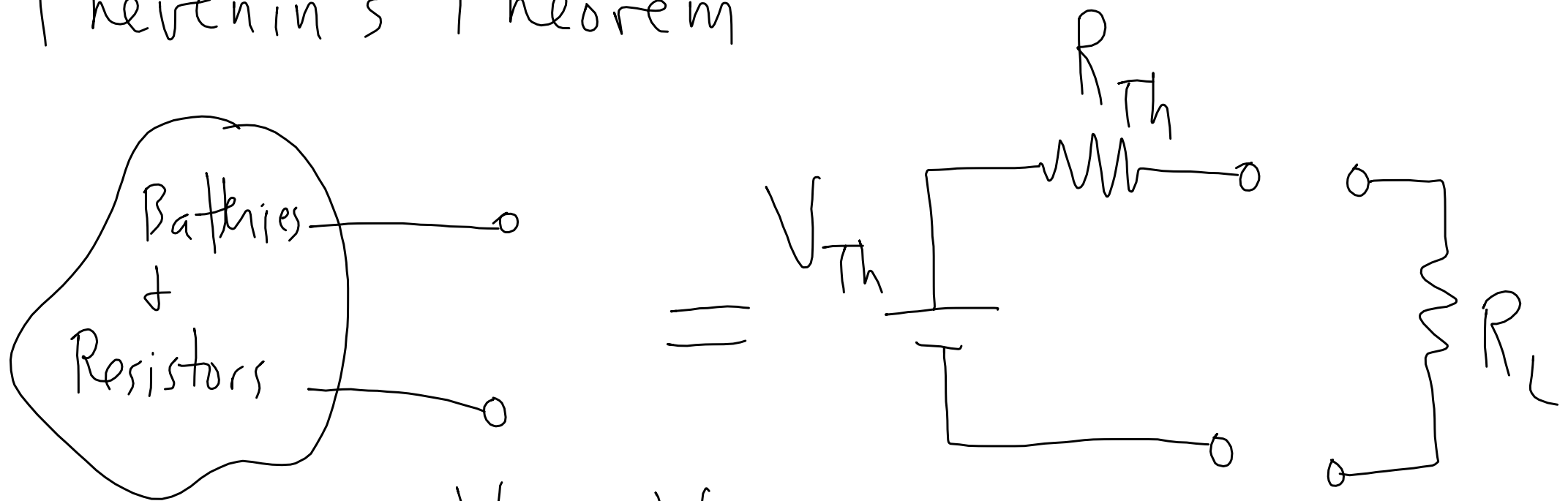


$$V_{Th} = V_{\text{open circuit}}$$
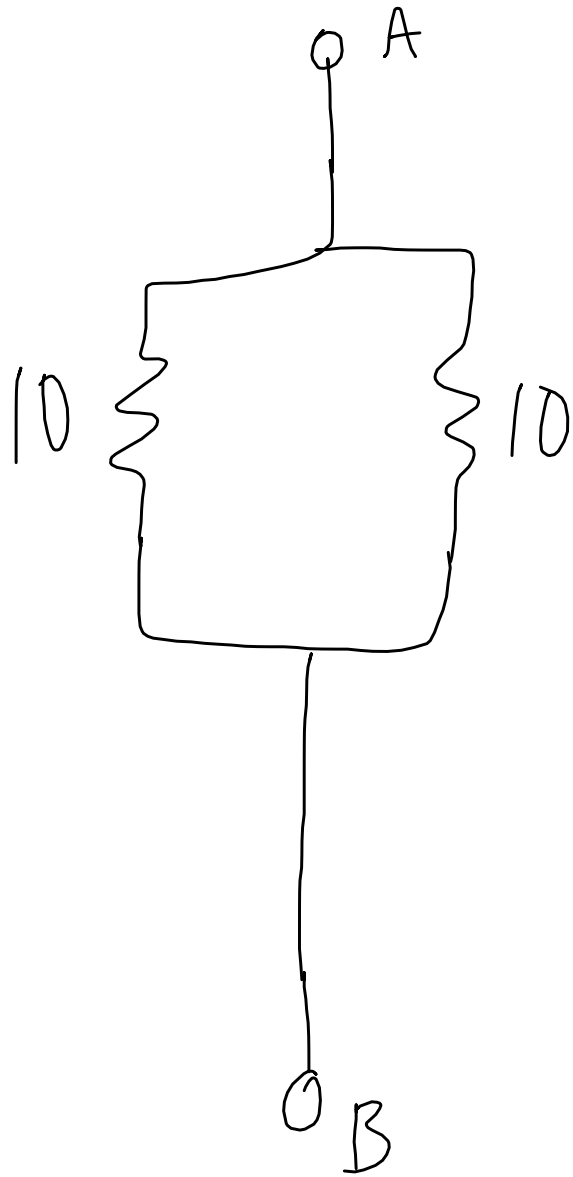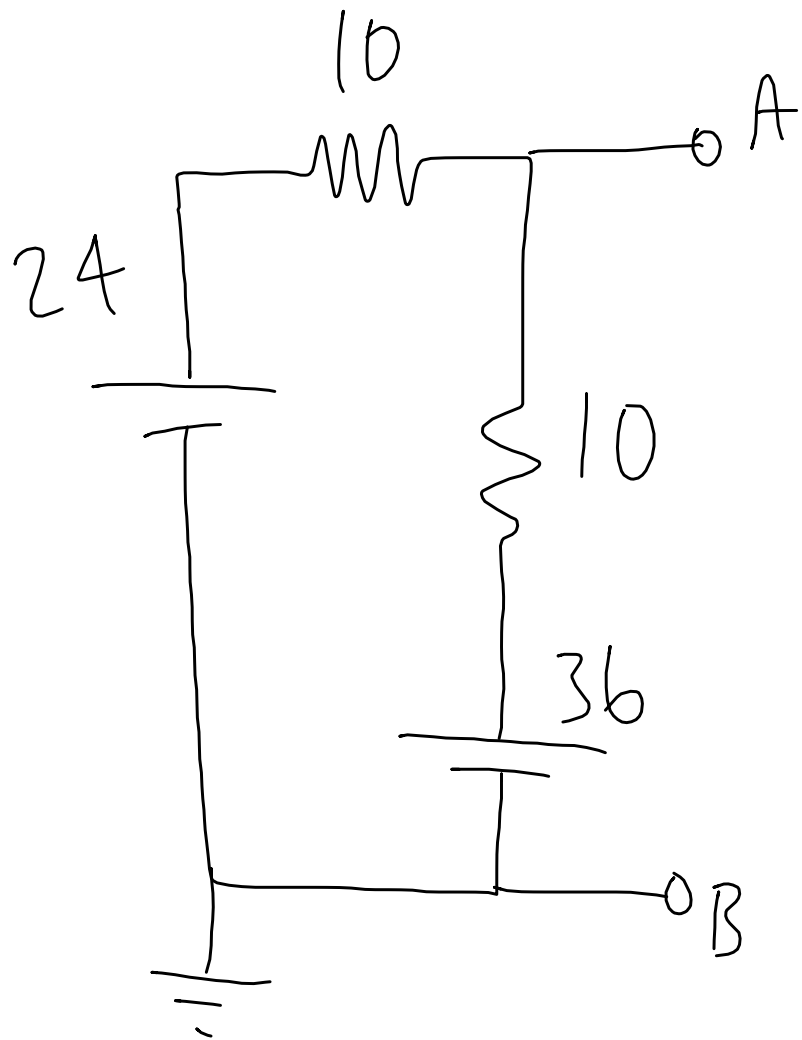
$$R_{Th} = R \text{ that world sees looking in} \\ \text{(with all batteries shorted) in}$$




$$R_{th} = 5 \Omega$$

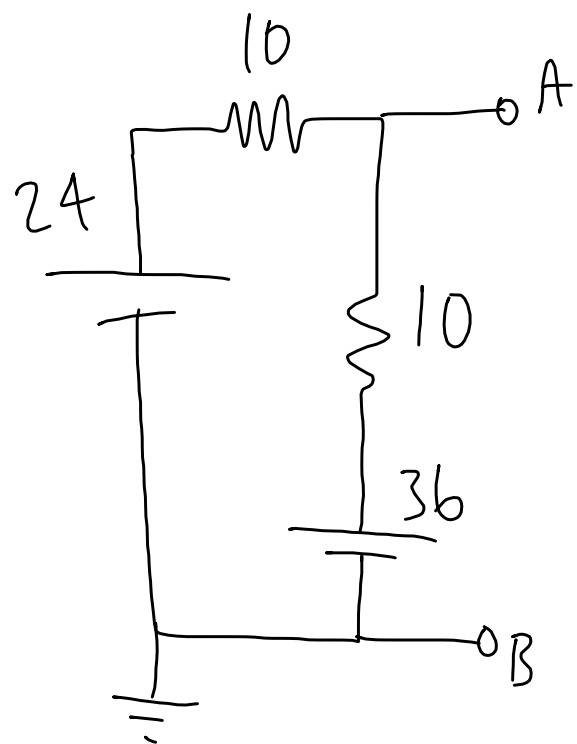

Use superposition to get V_A


1. Turn off 36V (short it)

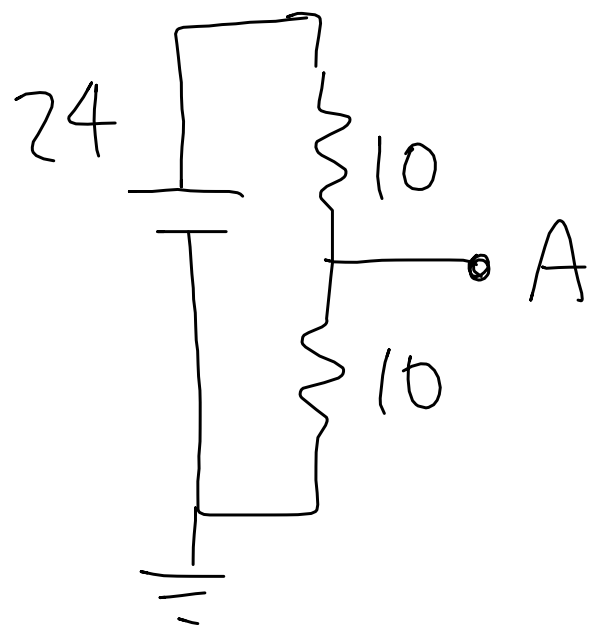

$$V_A = 12V$$

(just from 24V source)


2. Turn off 24V, turn on 36V

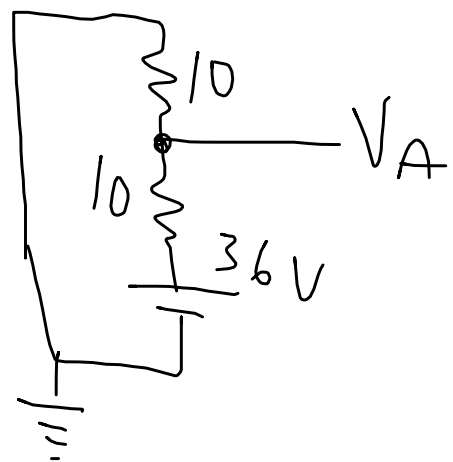

$$V_A = 18$$

Add them:

$$V_A = 30V$$

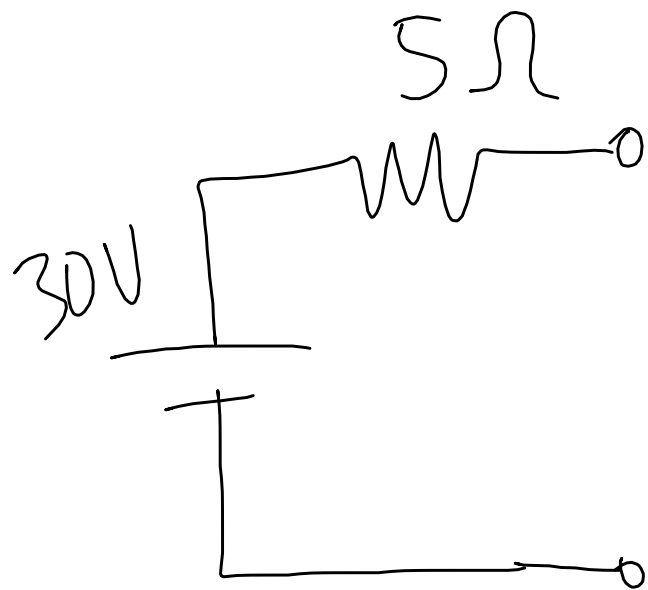

Capacitors

$$\frac{dV_c}{dt} = \frac{1}{C} \frac{dQ}{dt}$$

$$= \frac{I}{C}$$



$$C = \frac{Q}{V_c}$$

$$V_c = \frac{1}{C} \int i dt + \text{Const}$$

Suppose $I(t) = I_p \sin(\omega t)$ $\omega = 2\pi f$

$$V_c = \frac{1}{C} \int I_p \sin \omega t \, dt + \text{Const}$$

$$= -\frac{1}{\omega C} I_p \cos \omega t + \text{const}$$

$$= \frac{1}{\omega C} I_p \sin\left(\omega t - \frac{\pi}{4}\right) + \text{const}$$



If capacitor is ohmic...

$$R_c = \frac{V_c}{I_c} = \frac{-\frac{1}{\omega C} I_p \cos \omega t}{I_p \sin \omega t}$$

$$= -\frac{1}{\omega C} \tan \omega t ?$$

No phase info in this approach!