
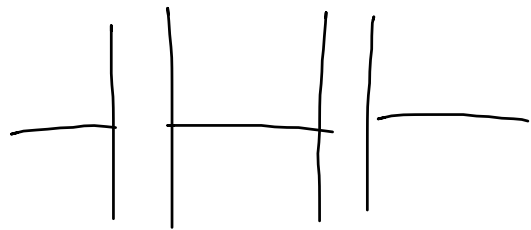


Capacitors

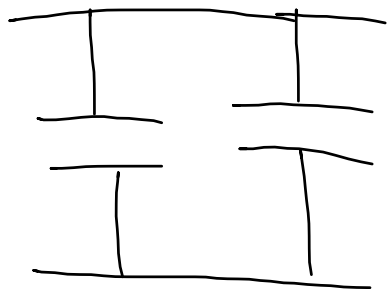


in series, $\frac{1}{C_{eg}} = \frac{1}{C_1} + \frac{1}{C_2}$

or $C_{eg} = \frac{C_1 C_2}{C_1 + C_2}$



$C_{eg} = C_1 + C_2$

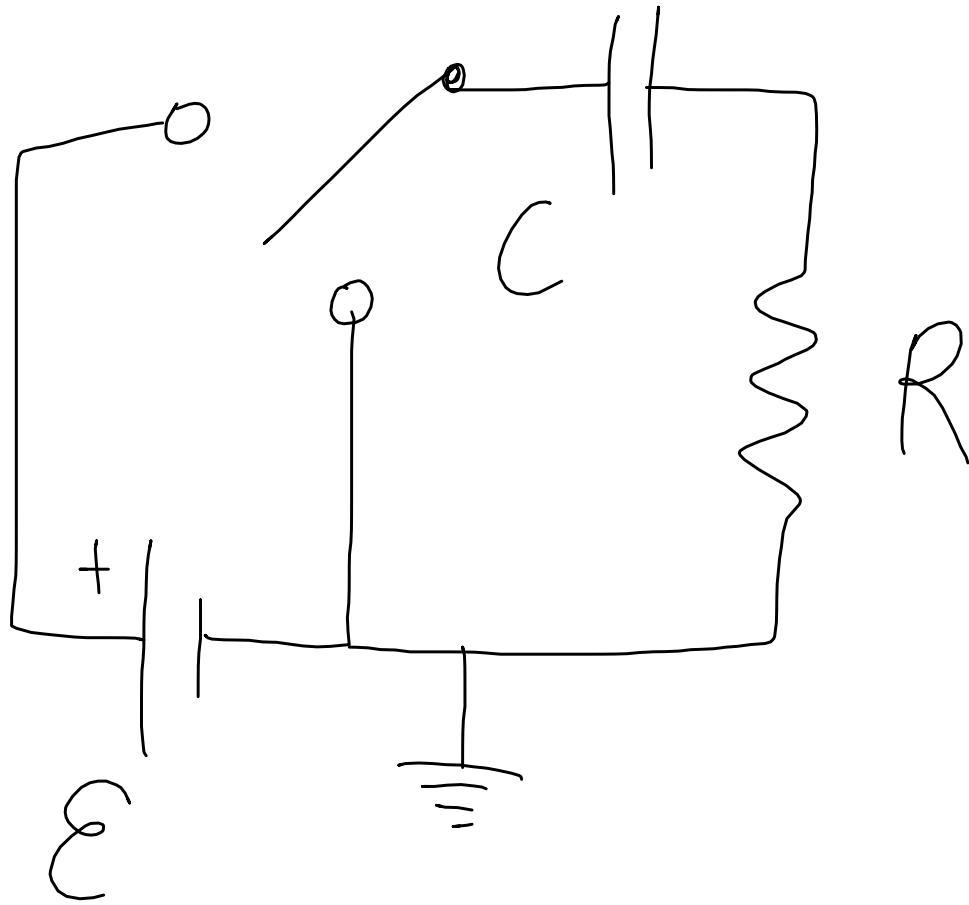

Recall

$$I = \frac{dQ}{dt}$$

First, charge...

$$\varepsilon - \frac{Q(t)}{C} - I(t)R = 0$$

$$\frac{dQ}{dt} = \frac{\varepsilon}{R} - \frac{Q(t)}{RC}$$

$$\frac{dQ}{dt} = - \left[\frac{Q(t) - C\mathcal{E}}{RC} \right]$$

$$\int_0^Q \frac{dQ}{Q - C\mathcal{E}} = - \int_0^t \frac{dt}{RC}$$


$$\ln(Q - C\mathcal{E}) \Big|_0^Q = - \frac{t}{RC} \Big|_0^t$$

$$\ln(Q - C\varepsilon) - \ln(-C\varepsilon) = -t/RC$$

$$\ln\left(\frac{Q - C\varepsilon}{-C\varepsilon}\right) = -t/RC$$

$$\frac{Q - C\varepsilon}{-C\varepsilon} = e^{-t/RC}$$
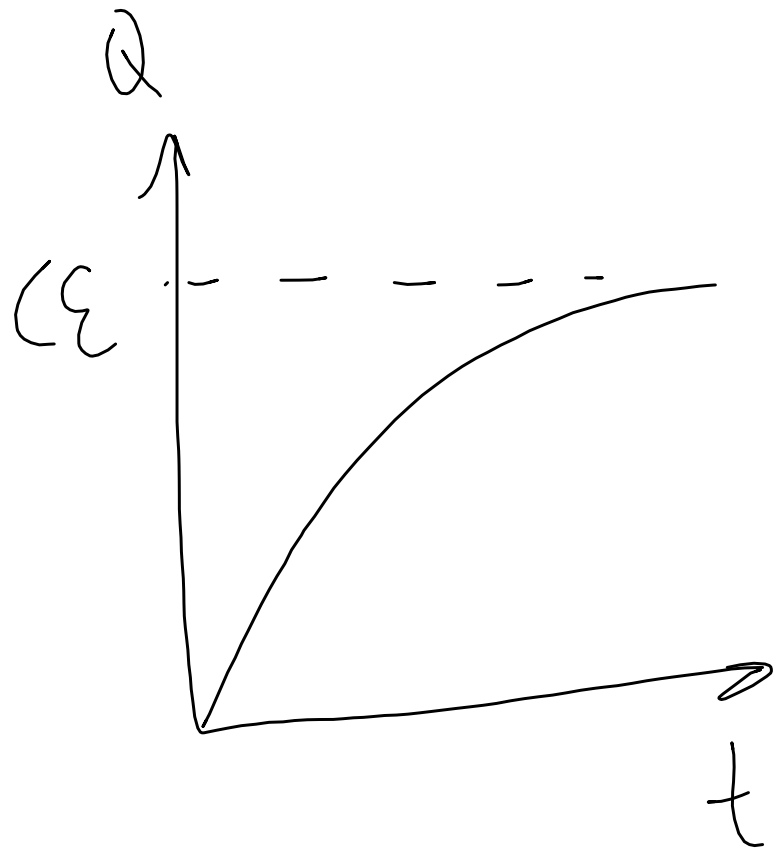
$$Q = C\varepsilon \left[1 - e^{-t/RC} \right]$$



$$I = \frac{dQ}{dt} = \frac{\mathcal{E}}{R} e^{-t/RC}$$

Discharge:

$RC = \text{time}$

$$V_c = \mathcal{E} e^{-t/RC}$$

$$I = \frac{\mathcal{E}}{R} e^{-t/RC}$$