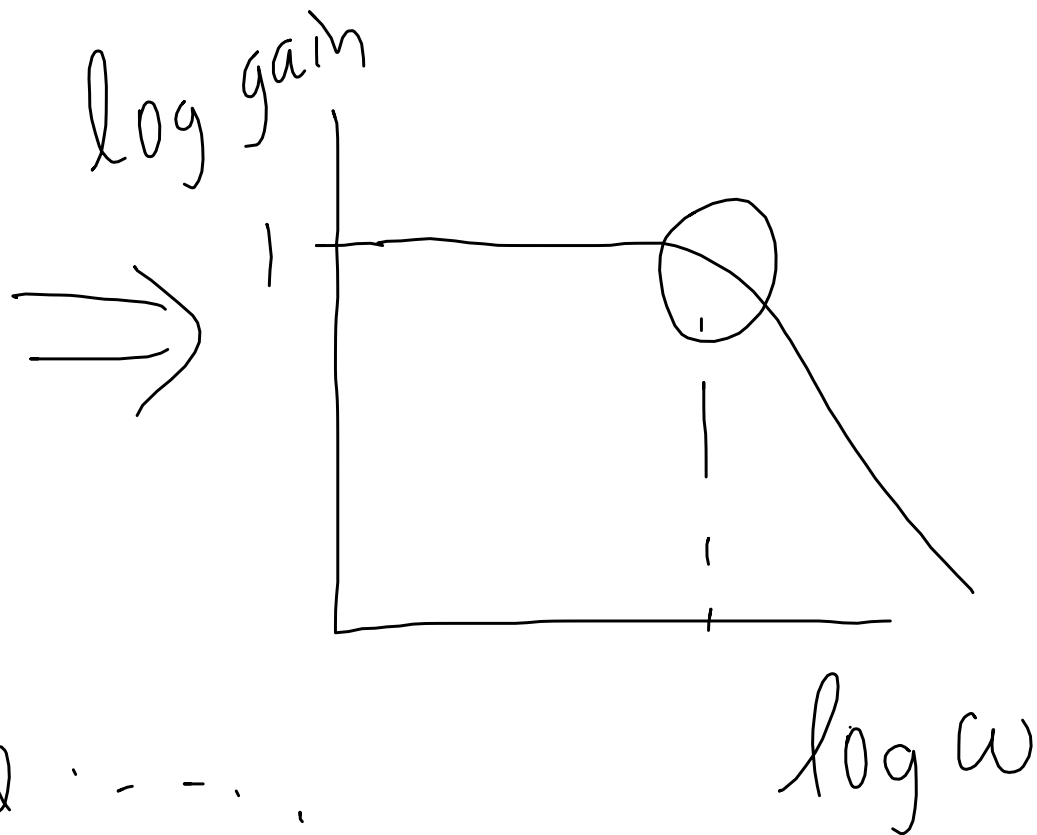


$$\frac{V_{out}}{V_{in}} = \frac{-i/\omega C}{R - \frac{i}{\omega C}} \Rightarrow \frac{1 - i\omega RC}{(\omega RC)^2 + 1}$$

$$\frac{1 - i\omega RC}{(\omega RC)^2 + 1} \Rightarrow \frac{\sqrt{1 + (\omega RC)^2}}{1 + (\omega RC)^2}$$

$$\Rightarrow \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

gain



Aside

$$\text{Bell} \Rightarrow \log\left(\frac{P_{\text{out}}}{P_{\text{in}}}\right) \Rightarrow \text{"bel"}$$

$$10 \log\left(\frac{P_{\text{out}}}{P_{\text{in}}}\right) \Rightarrow \text{decibel}$$

Recall $P = \frac{V^2}{R}$ for resistor



$$10 \log \frac{V_{\text{out}}^2}{V_{\text{in}}^2} = 20 \log\left(\frac{V_{\text{out}}}{V_{\text{in}}}\right) \quad \swarrow \text{Bode plot}$$

So @ "half power point"

$$\frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{2}} \quad (\text{since } P \propto V^2)$$

So

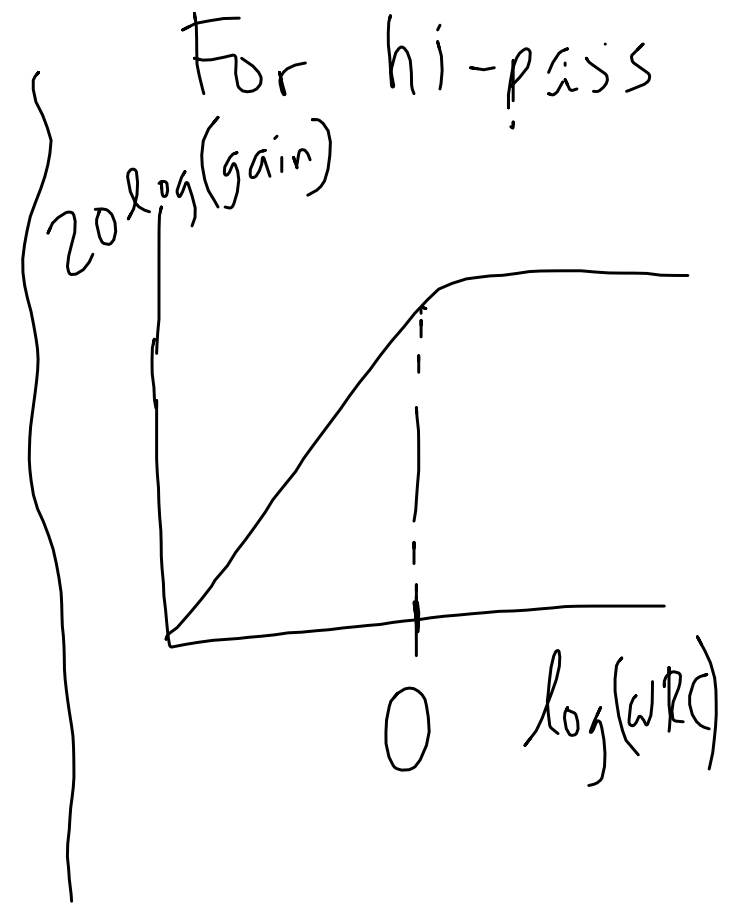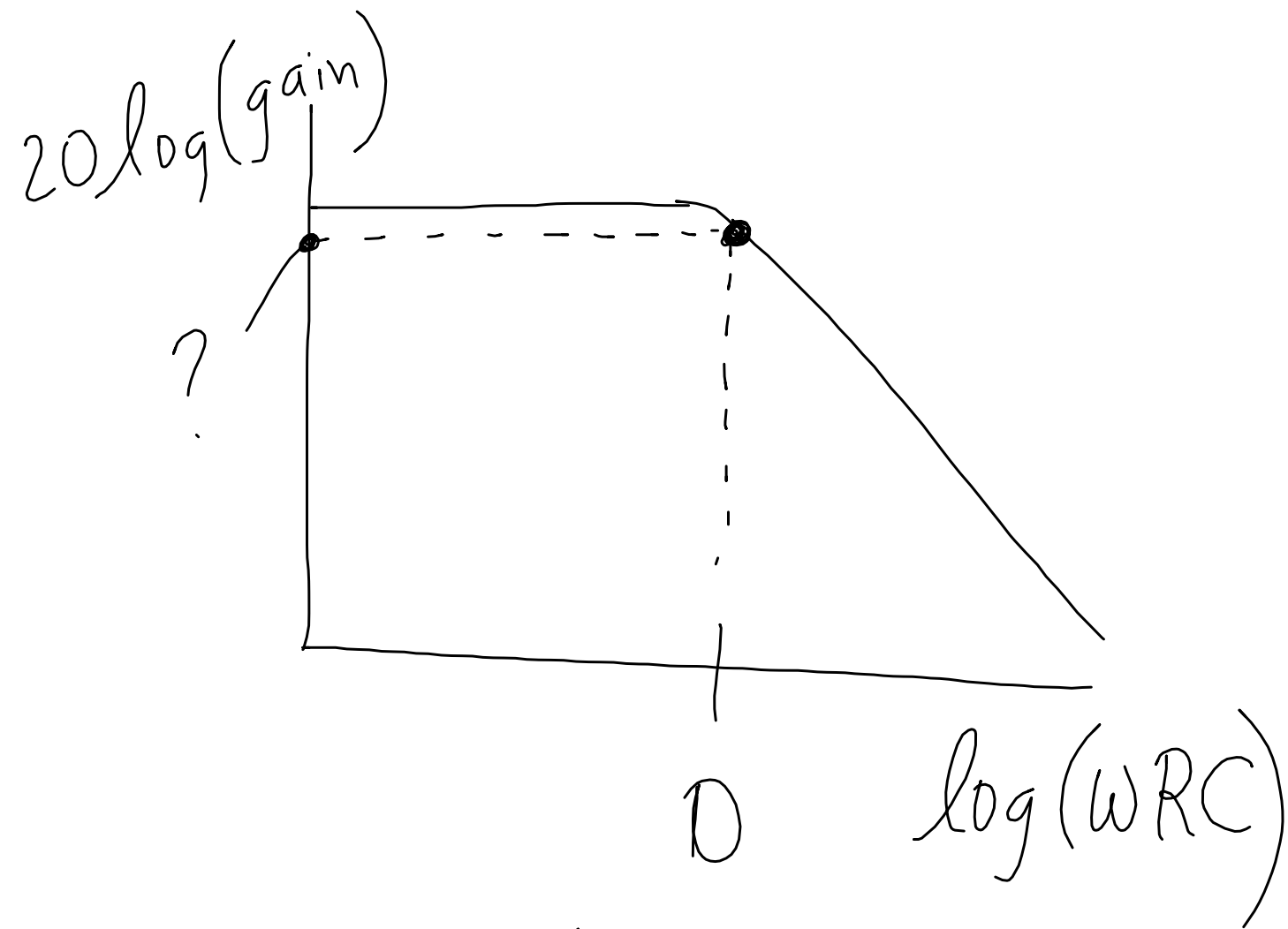
$$\frac{1}{\sqrt{1 + (\omega RC)^2}} = \frac{1}{\sqrt{2}} \quad \text{when } \omega = \frac{1}{RC}$$



$$20 \log\left(\frac{1}{\sqrt{2}}\right) = -3.01 \text{ dBV}$$

$$\frac{V_{out}}{V_{in}} = \frac{1 - i\omega RC}{(\omega RC)^2 + 1}$$

for low pass

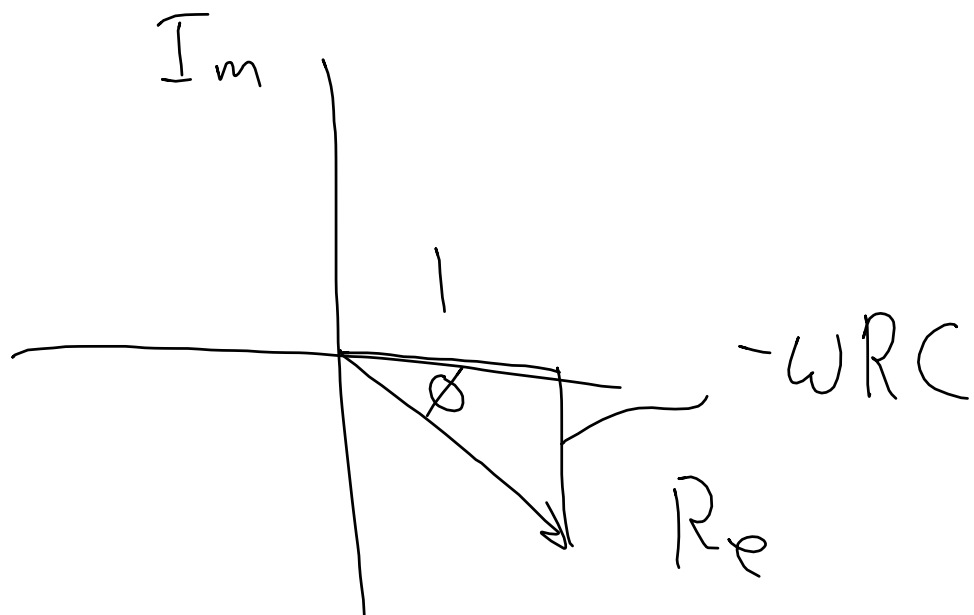

$$\phi = \tan^{-1} \left(\frac{-\omega RC}{1} \right)$$

$$= -\tan^{-1}(\omega RC)$$