

Make a voltage change  
at the base  $\Rightarrow \Delta V_B$

Follower  $\Rightarrow \Delta V_E = \Delta V_B$

Then 
$$\Delta I_E = \frac{\Delta V_E}{R} = \frac{\Delta V_B}{R}$$

$$I_E = I_B + I_C = I_B + \beta I_B$$


$$I_E = (\beta + 1) I_B$$

$$\Delta I_B = \frac{\Delta I_E}{\beta + 1}$$

$$\Delta I_B = \frac{\Delta V_B}{R(\beta + 1)} \Rightarrow$$

$$\frac{\Delta V_B}{\Delta I_B} = R(\beta + 1)$$

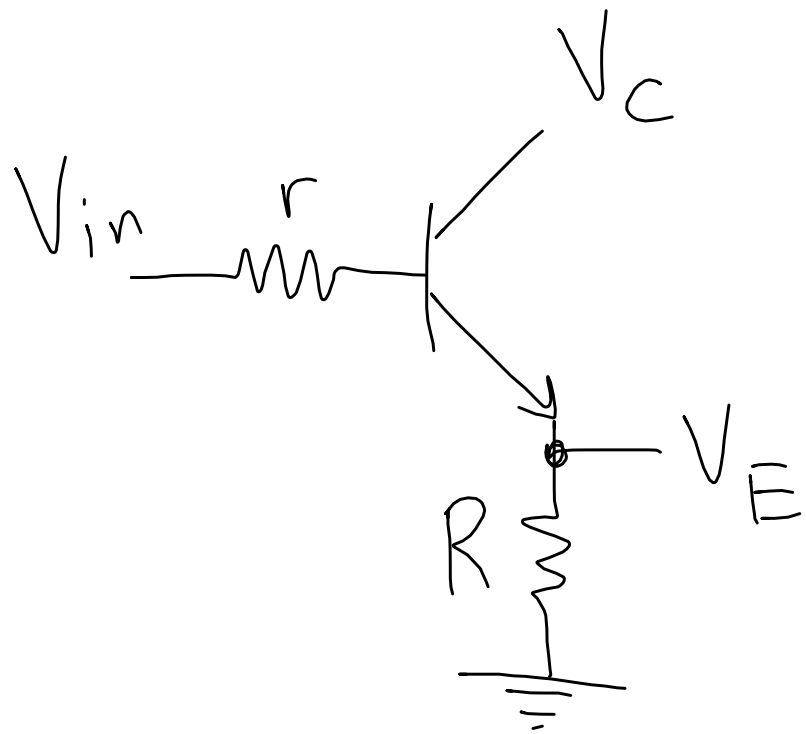input impedance  
of the  
transistor  
(follower)



By KVL

$$V_{in} - I_B r - 0.7 - V_E = 0$$

$$V_{in} = I_B r + 0.7 + V_E$$

$$\Delta V_{in} = (\Delta I_B) r + \Delta V_E$$

Assume that  $V_{in} = \text{const} \Rightarrow \Delta V_{in} = 0$

$$\Delta I_B = - \frac{\Delta V_E}{r}$$

$$\Delta I_B = - \frac{\Delta V_E}{r}$$

Recall  $I_B = I_E - I_C$



$$I_E = (\beta + 1) I_B$$

$$\Delta I_E = (\beta + 1) \Delta I_B$$

$$\Delta I_B = \frac{\Delta I_E}{\beta + 1} = - \frac{\Delta V_E}{r}$$

$$\frac{\Delta V_E}{\Delta I_E} = - \frac{r}{\beta + 1}$$

output impedance  
of our follower

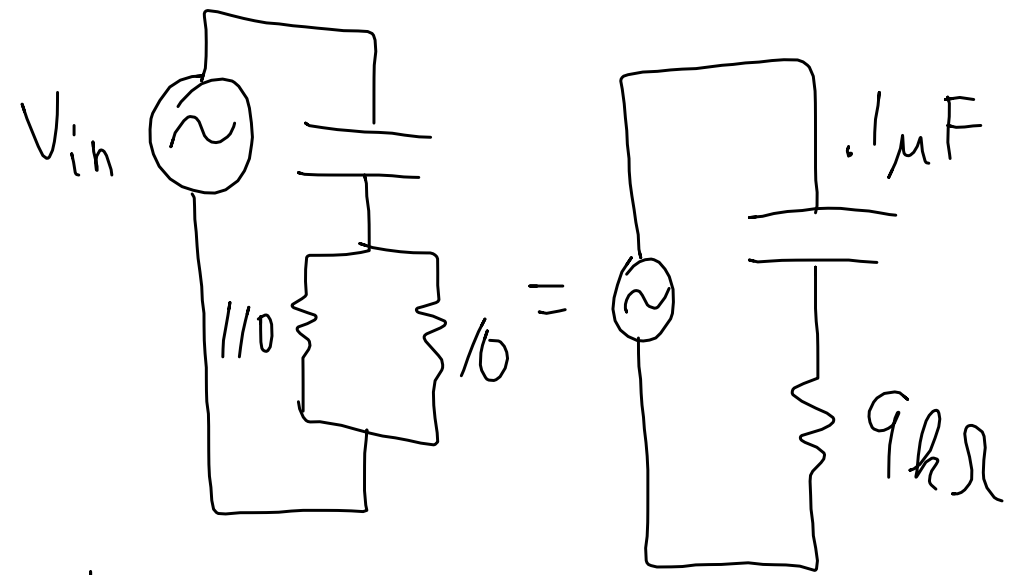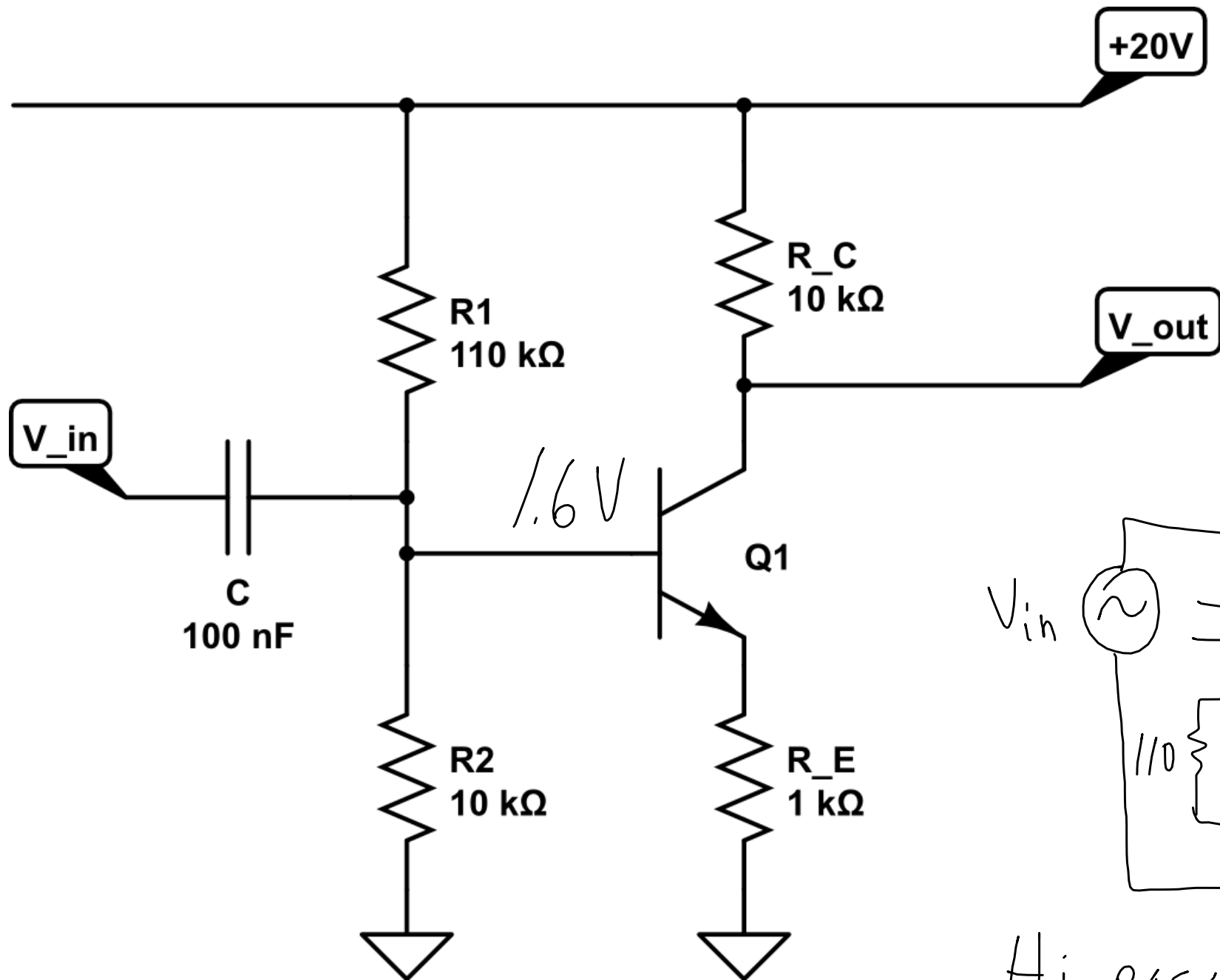

Hi pass filter

$f > 170 \text{ Hz}$  will pass  
 $\omega_0 \approx \frac{1}{(9 \times 10^3)(0.1 \times 10^{-6})} \approx 1 \text{ kHz}$

Suppose "wiggle"  $V_B$  appears at base


Emitter follower  $\Rightarrow$  same  $V_E$


Emitter current  $\Rightarrow i_E = \frac{V_E}{R_E} = \frac{V_B}{R_E}$

$\downarrow$   
 $\approx i_C$

$$V_C = -i_C R_C = -\frac{V_B}{R_E} R_C = -V_B \frac{R_C}{R_E}$$

$$\frac{V_C}{V_B} = -\frac{R_C}{R_E}$$

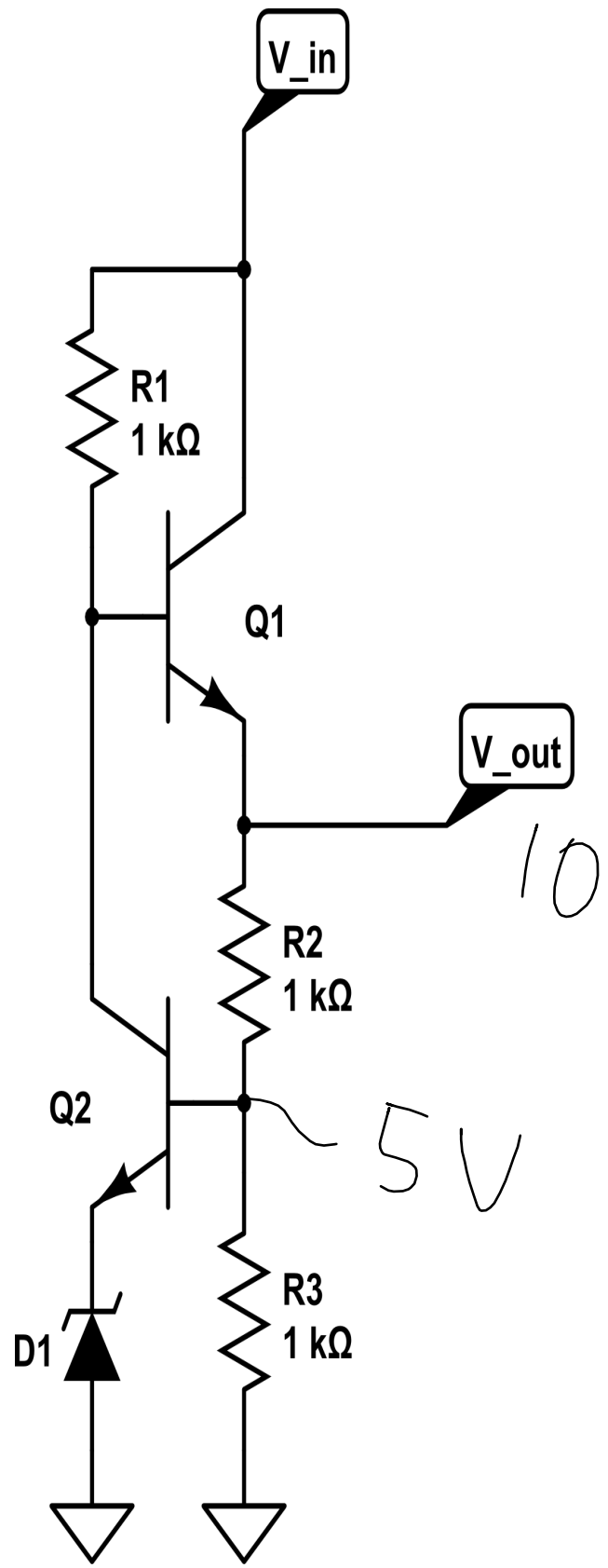


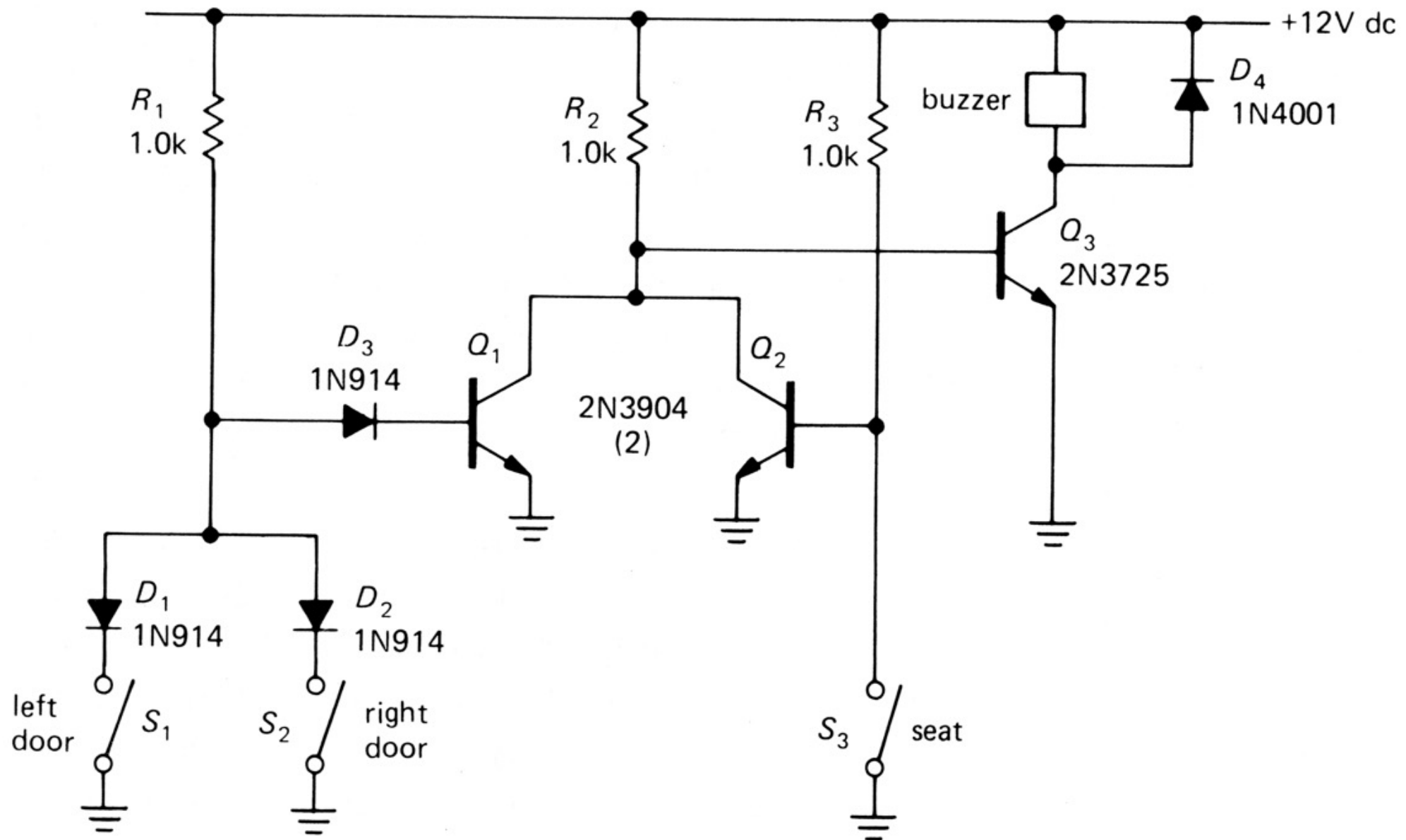



# The Promised Land....

## Operational Amplifiers

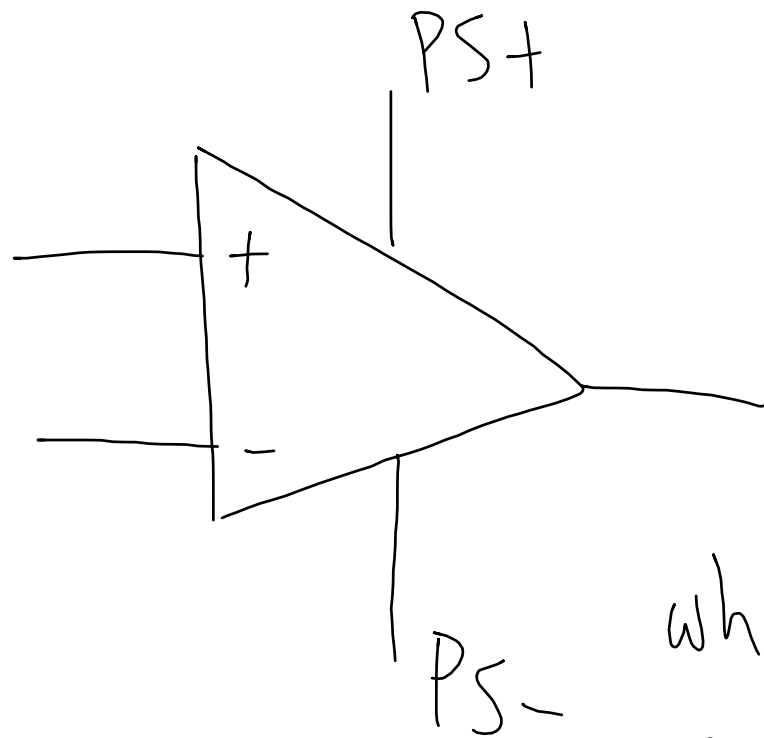

Rule #1. No current flows into inputs

Rule #2: Output does whatever it can to make input voltages equal