
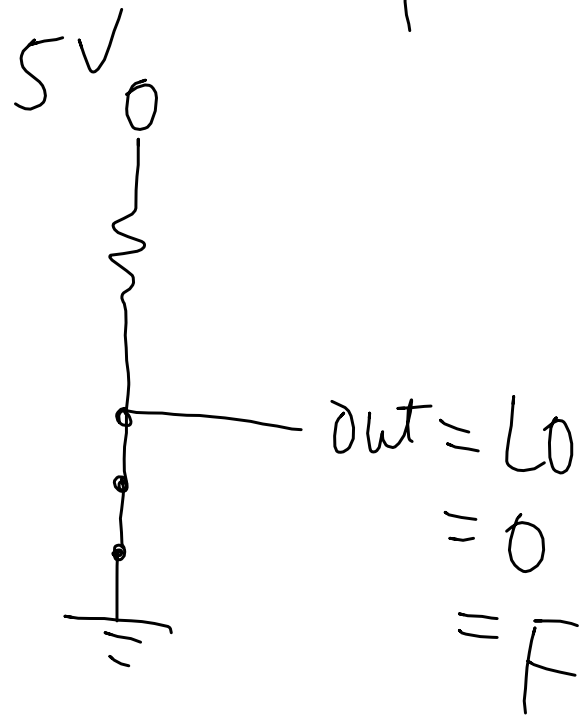


Digital Electronics

Two states: HI LOW
 1 0
 T F

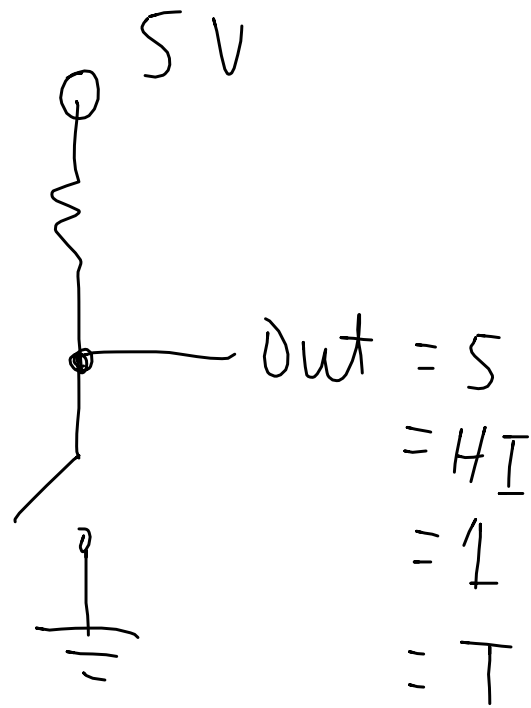

Replace switch
w/ transistor
& $V_{01}a^-$

The math

Binary \Rightarrow 0, +1 \Rightarrow base 2

Octal \Rightarrow 0 \rightarrow 7 \Rightarrow base 8

Hexadecimal \Rightarrow (0 \rightarrow 15) \rightarrow 0-9, A \rightarrow F \Rightarrow base 16

$$\begin{array}{r} 1 \\ + 1 \\ \hline 10 \end{array}$$

$$\begin{array}{r} 101 \\ + 011 \\ \hline 1000 \end{array}$$

What about subtraction?

2 ways: Sign bit

$$0101 = 5$$

$$\textcircled{1}101 = -5$$

$$\begin{array}{r} 0101 \quad 5 \\ + 1101 \quad -5 \\ \hline 10010 = 2 \end{array}$$

Bad

Second way:

101 \Rightarrow 5
 ↙
 010 one's complement

+ 1


011 two's complement

101
+ 011

1000

Terminology:


0, 1 \Rightarrow bits

01010101 \Rightarrow byte
 nibble

Moving them:

1. Serial - one bit after another
2. Parallel - all n bits at once


Logic Gates

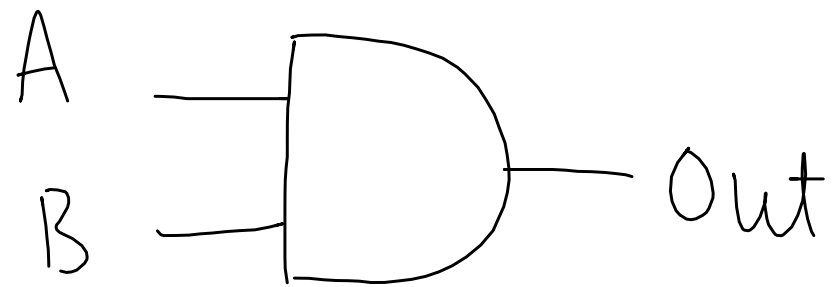

A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

AND



$A \cdot B$

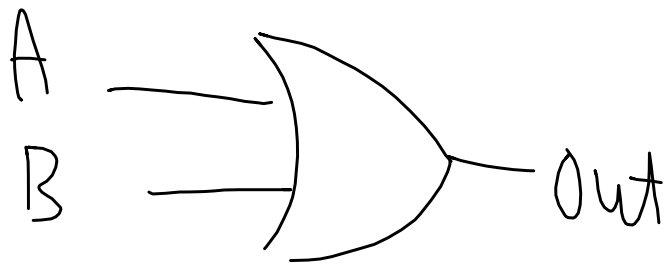


A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1

OR

$A + B$

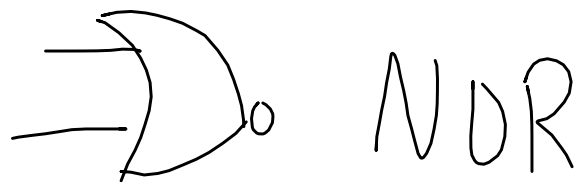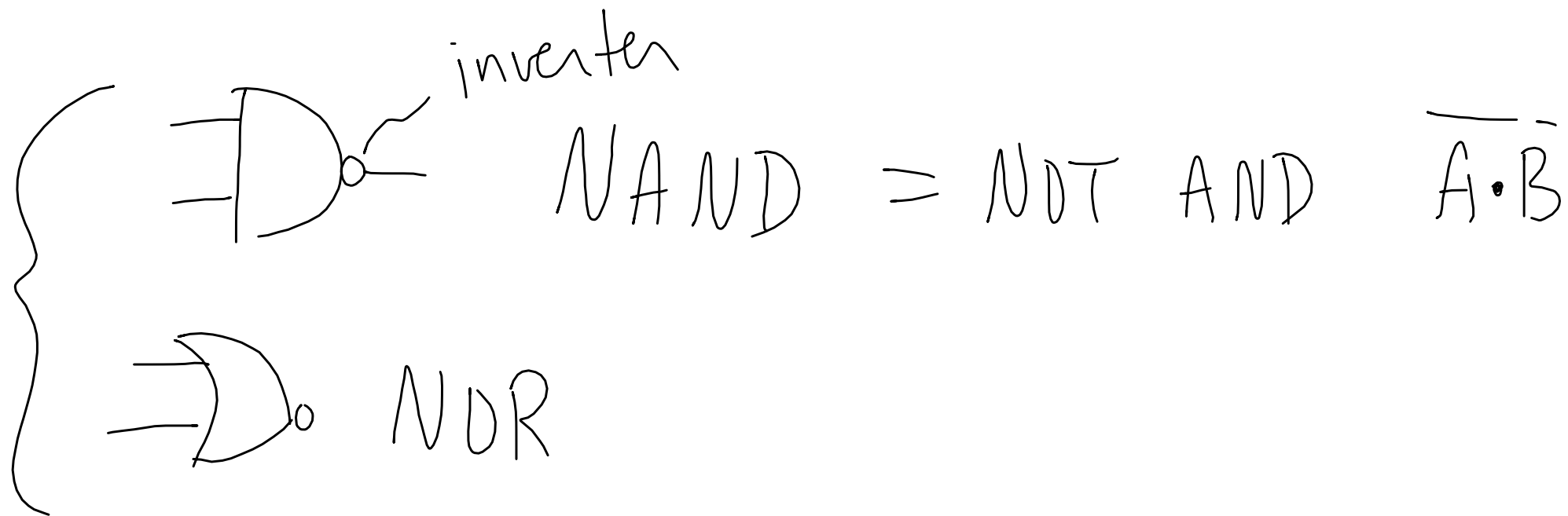


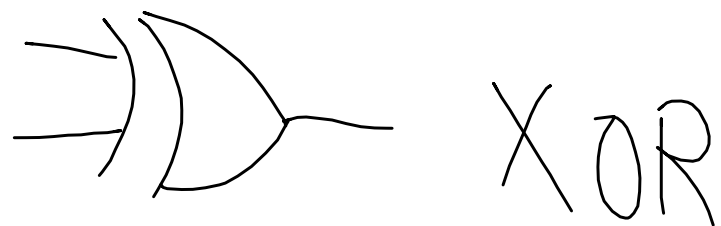Can make any 2-input gate from
 combination of NANDs, NORs, & inverters



A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

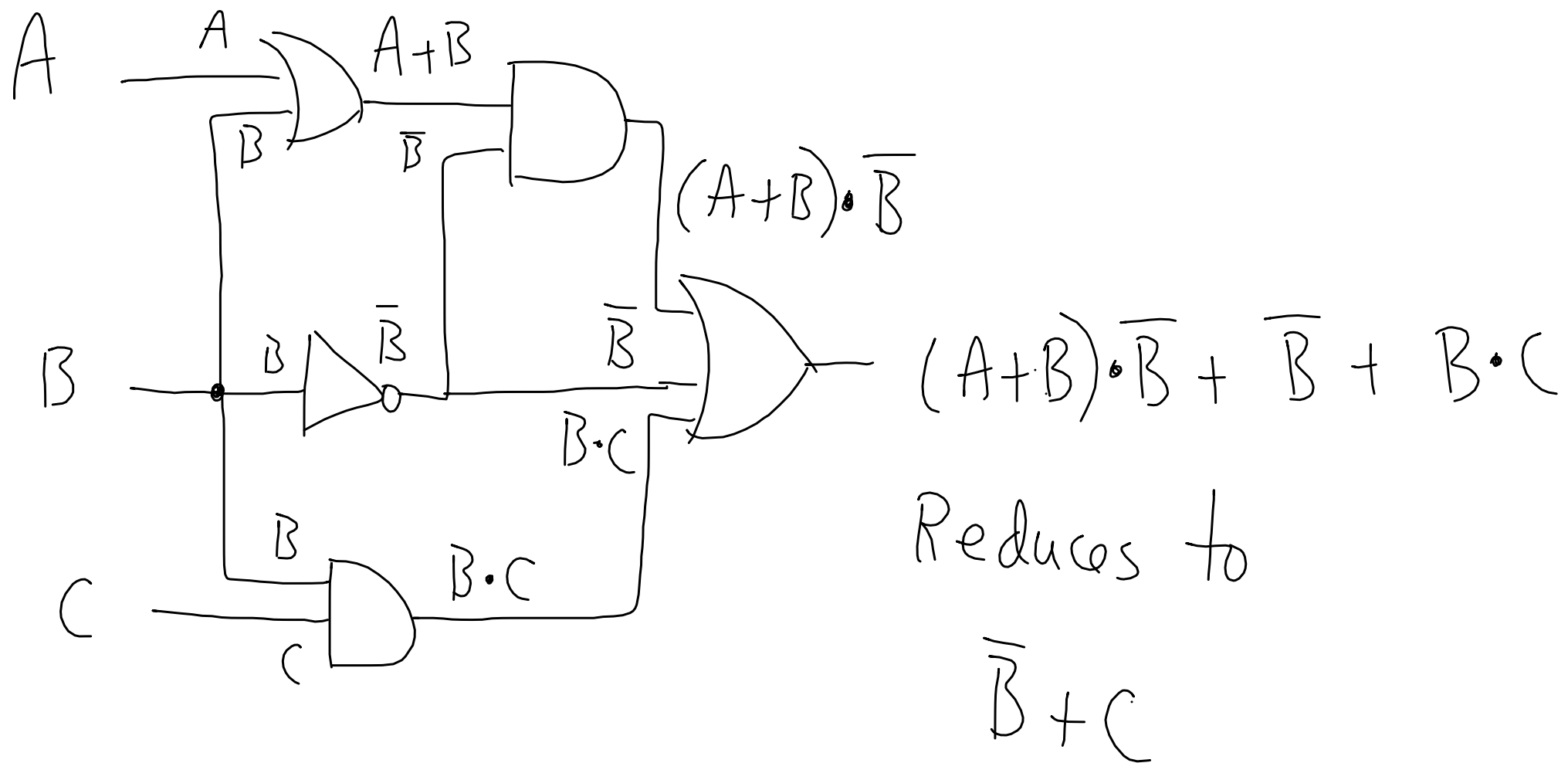There are theorems that help
simplify the logic






One handy theorem!

De Morgan's theorem


$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

$$\downarrow \quad \overline{A + B} = \bar{A} \cdot \bar{B}$$

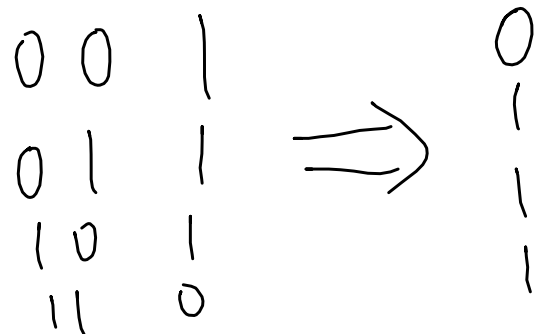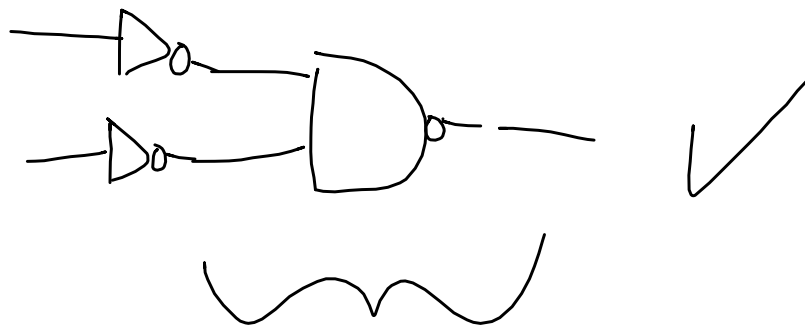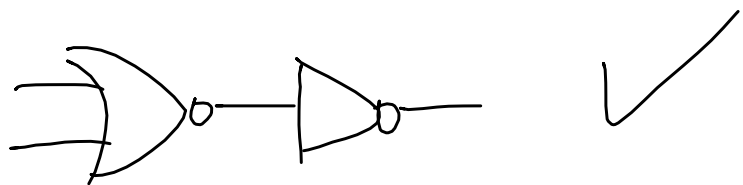Try this: using only NANDS, NORs + inverters,
make an OR gate




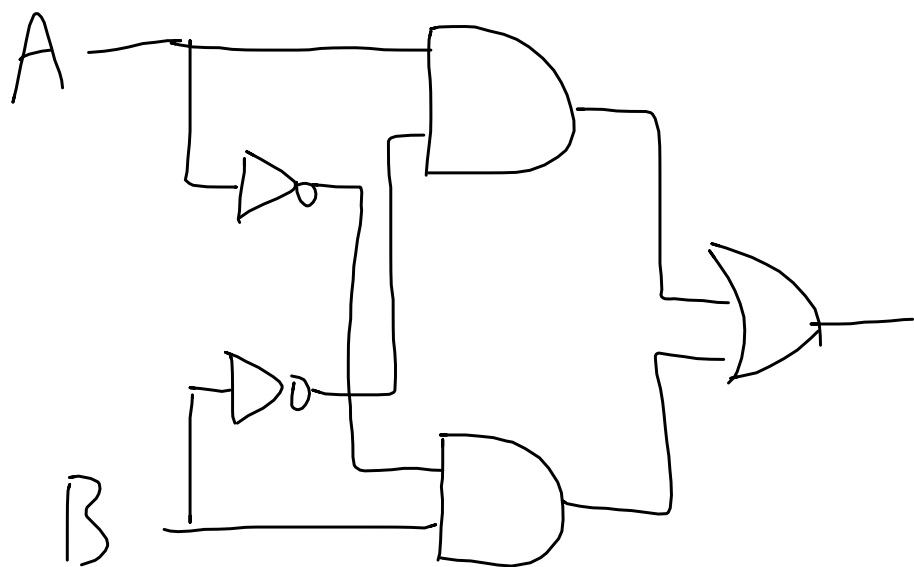
Sometimes you see the result best in a truth table



A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

It's an
XOR

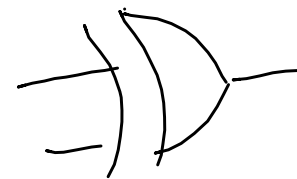

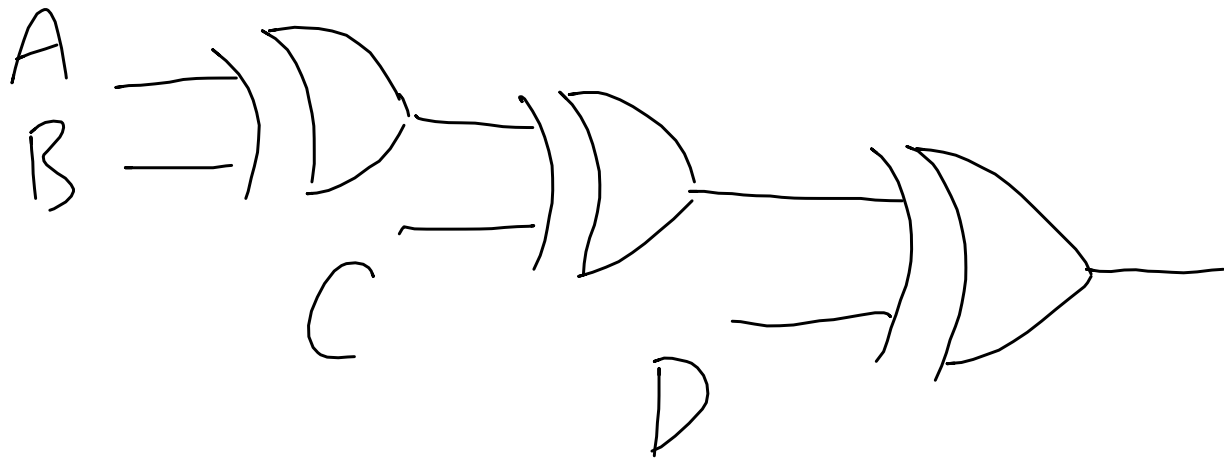


Parity

0 or even # of 1's \Rightarrow 0
 odd # " " \Rightarrow 1

A	B	C	D	Out
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1

More moving bits around

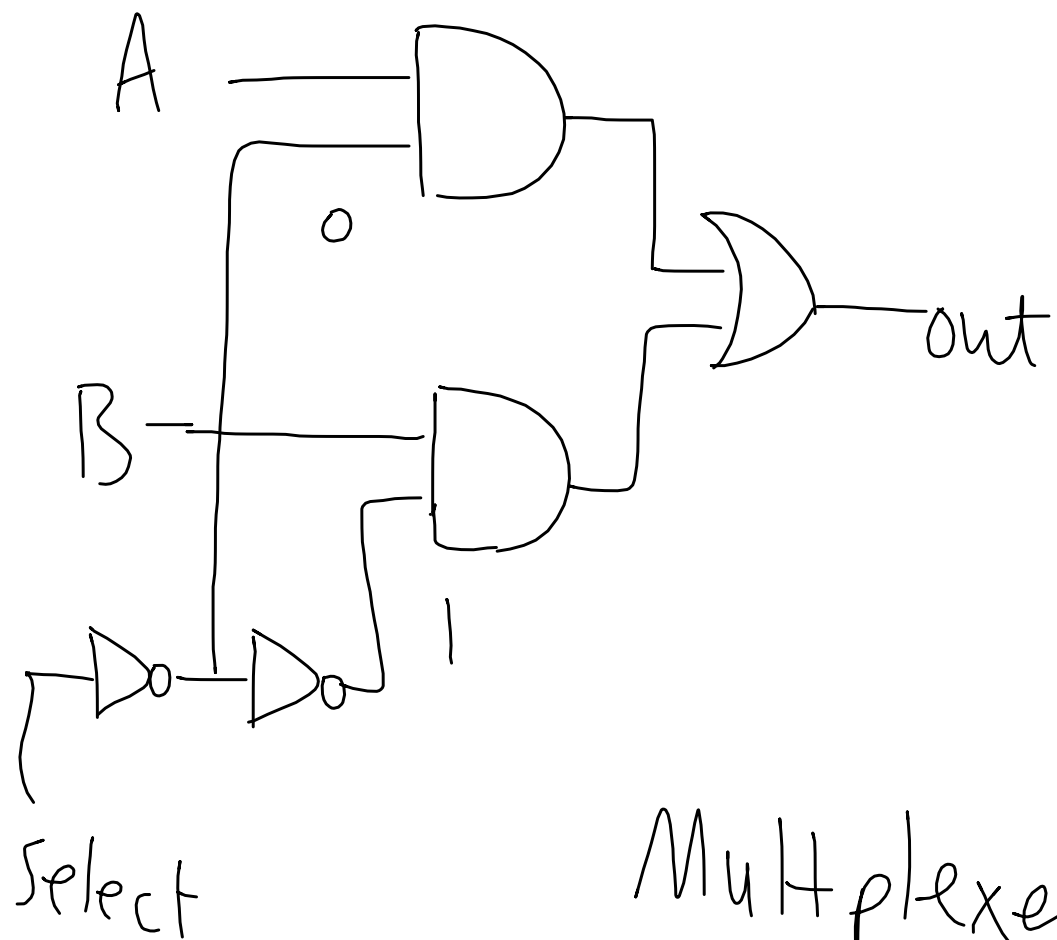

Multiplexer
(+ decoders)


If select = 0,

$$\text{out} = A$$

If select = 1,

$$\text{out} = B$$

Example \Rightarrow 7-segment LED

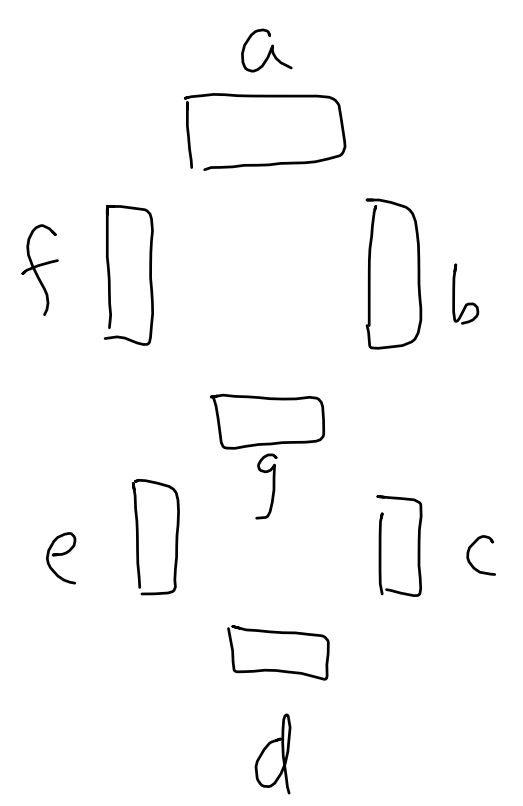

Write a "2"

Turn on a, b, d, e, g

10 possible "numbers"

Needs 4 bits of info

0010 \Rightarrow "2"