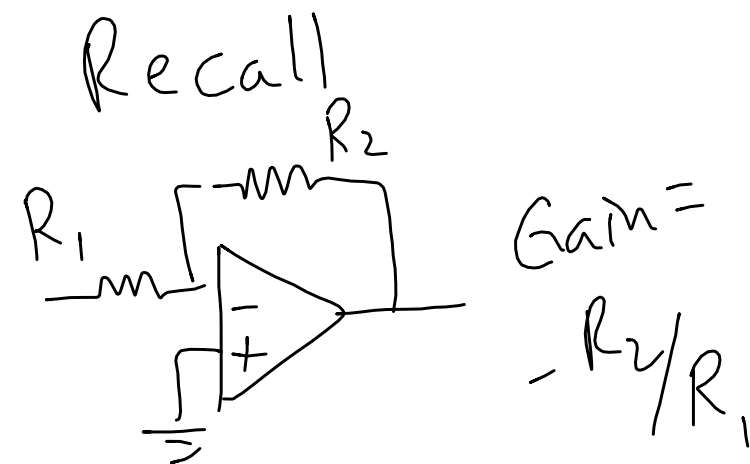


Assume V_{in} is AC

$$\text{Gain} = \frac{-Z_f}{Z_{in}}$$

$$Z_f = R_f \quad Z_{in} = R - \frac{i}{\omega C}$$

$$\text{Gain} = \frac{-R_f}{R - \frac{i}{\omega C}} \cdot \frac{R + \frac{i}{\omega C}}{R + \frac{i}{\omega C}} = \frac{-R_f R - \frac{i R_f}{\omega C}}{R^2 + \frac{1}{\omega^2 C^2}}$$



$$\text{Gain} = -\frac{R_f}{R} \frac{R^2 + \frac{iR}{\omega C}}{R^2 + \frac{1}{\omega^2 C^2}}$$


$$= -\frac{R_f}{R} \frac{1 + \frac{i}{\omega RC}}{1 + \frac{1}{\omega^2 R^2 C^2}}$$


Let $x = \omega RC$

$$= -\frac{R_f}{R} \frac{1 + i/x}{1 + 1/x^2}$$

Abs
value \rightarrow

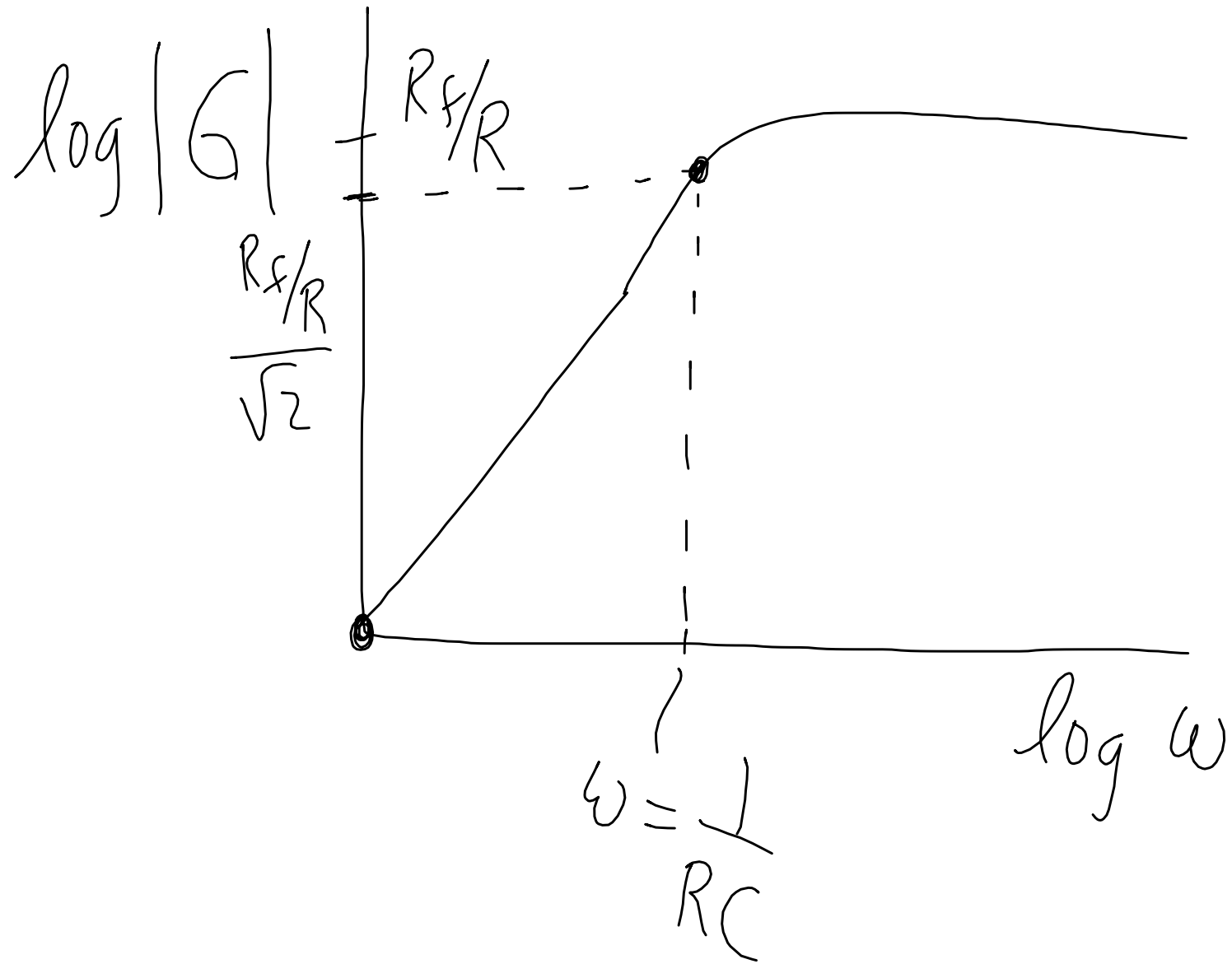
$$\frac{R_f}{R} \frac{\sqrt{1 + \frac{1}{x^2}}}{1 + \frac{1}{x^2}} = \frac{R_f/R}{\sqrt{1 + \frac{1}{x^2}}}$$



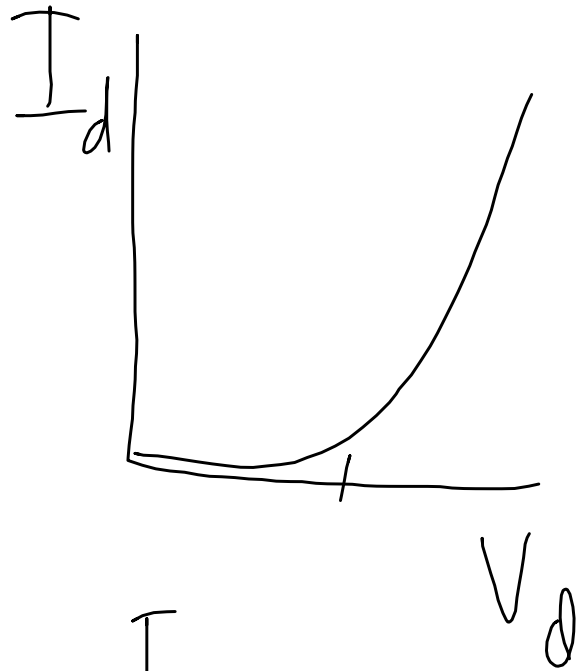

Ebers-Moll model
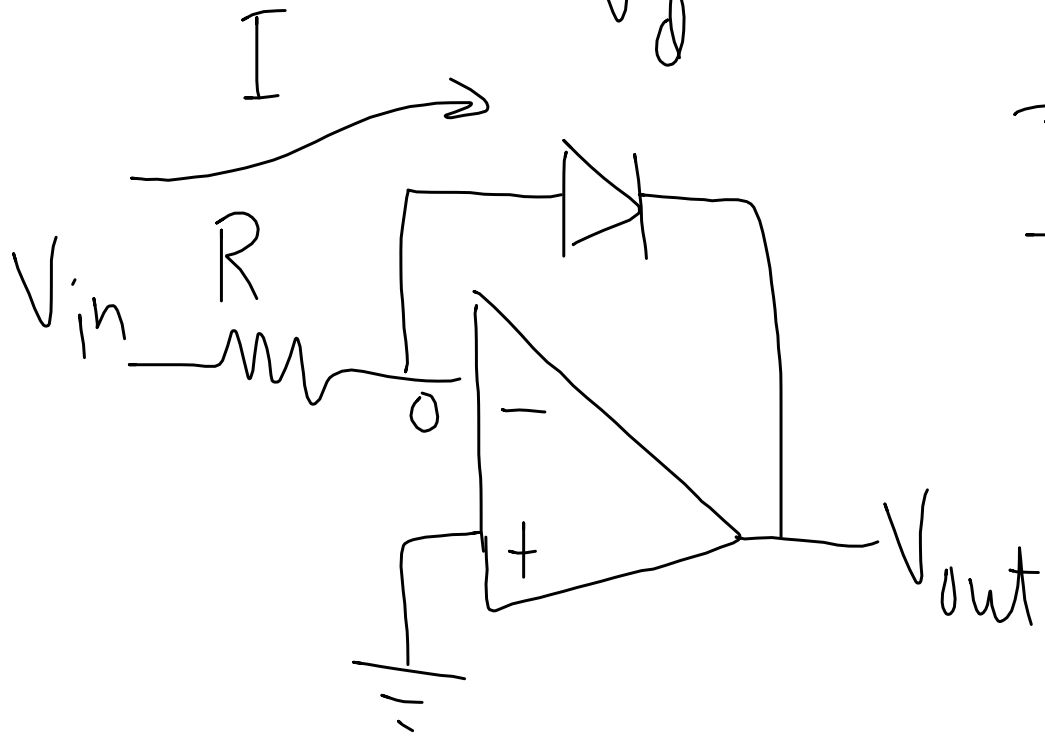
$$I_d \approx I_{sat} e^{V_d/V_T}, \quad V_T = \frac{k_B T}{e}$$



$$I = \frac{V_{in}}{R} = I_d$$

$$V_{out} = -V_d$$


$$I_d \approx I_{\text{sat}} e^{V_d/V_T}, \quad V_T = \frac{k_B T}{e}$$

$$V_d = V_T \ln \frac{I_d}{I_{\text{sat}}}$$

$$V_{\text{out}} = -V_T \ln \frac{I_d}{I_{\text{sat}}}$$

$$= V_T \left[\ln I_{\text{sat}} - \ln I_d \right] = V_T \left[\ln I_{\text{sat}} - \ln \frac{V_{\text{in}}}{R} \right]$$
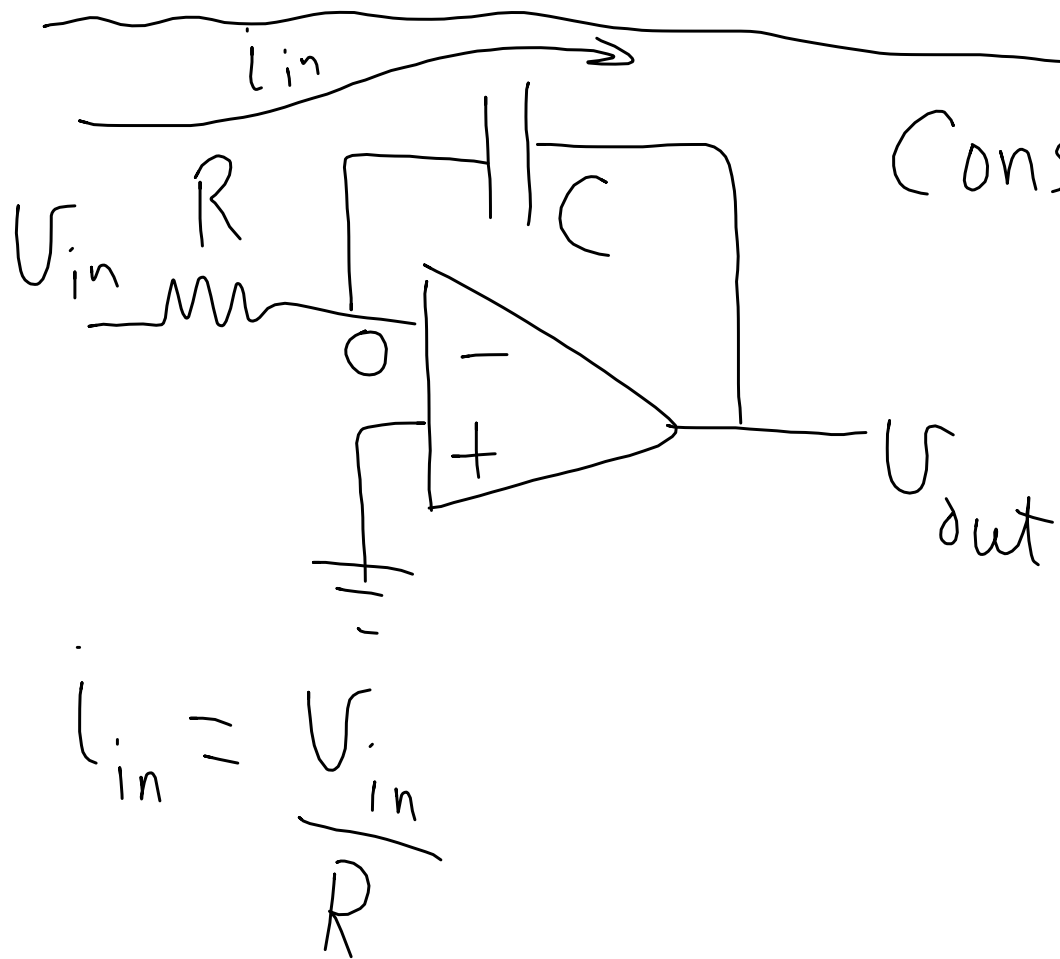
$$V_{out} = V_T \left[\ln I_{sat} - \ln \frac{V_{in}}{R} \right]$$



Consider $A(\omega) \Rightarrow$ lower case $V + i$

$$V_{out} = -V_C$$


$$= -\frac{q}{C}$$

$$\frac{dV_{out}}{dt} = \frac{-dq/dt}{C} = -\frac{I_{in}}{C}$$

$$\frac{dV_{out}}{dt} = -\frac{V_{in}}{RC}$$

$$V_{out} = -\frac{1}{RC} \int V_{in} dt + C$$

Integrator

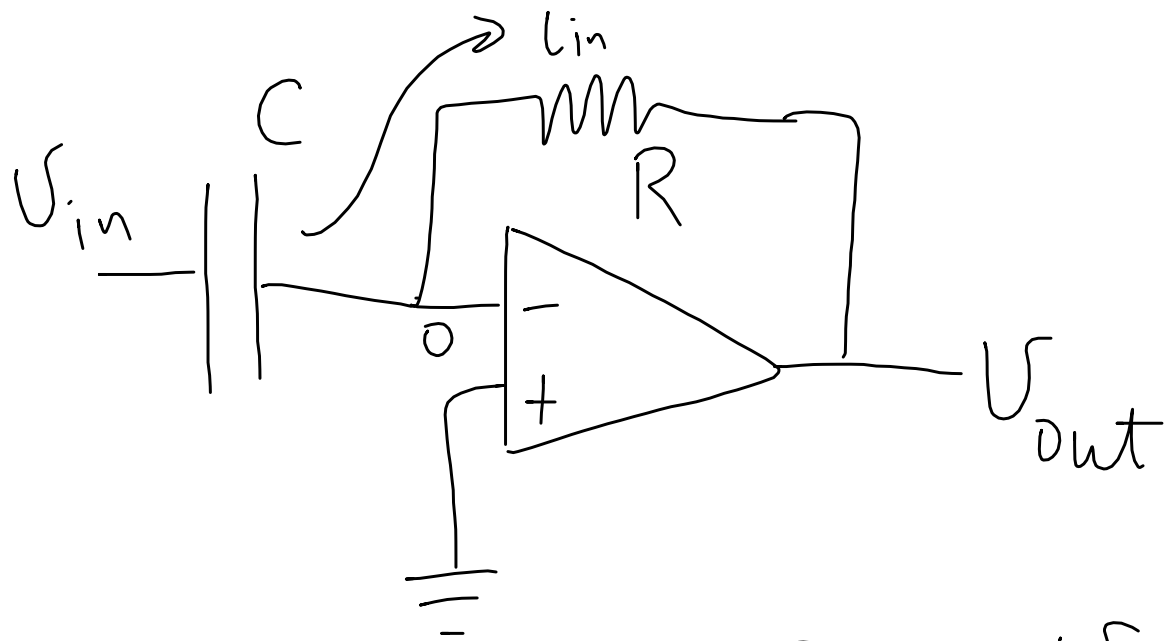



$$U_{out} = -i_{in} R$$


$$U_{in} = U_c = \frac{q}{C}$$

$$\frac{dU_{in}}{dt} = \frac{dq/dt}{C} = \frac{i_{in}}{C} = \frac{-U_{out}}{RC}$$


$$U_{out} = -RC \frac{dU_{in}}{dt} \quad \text{differentiator}$$

Suppose we construct

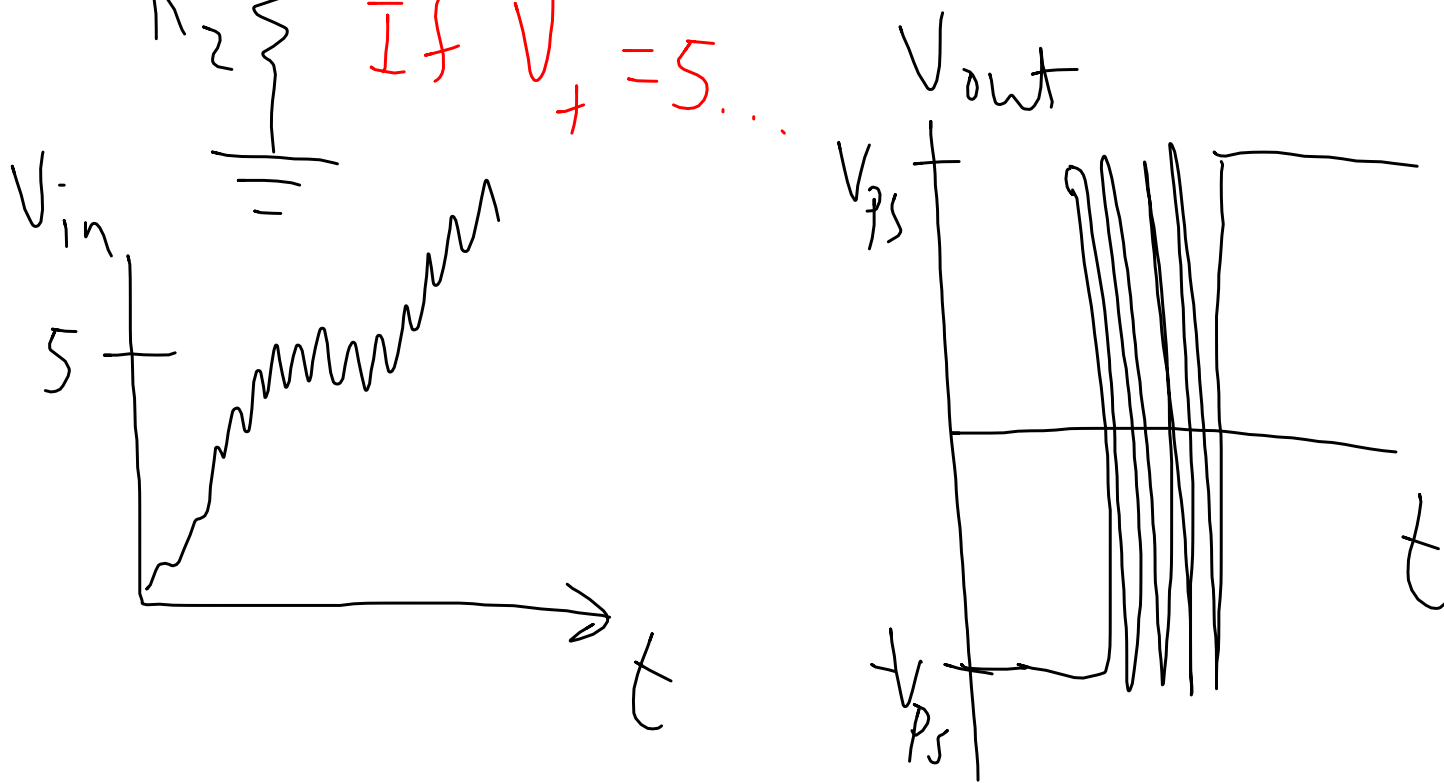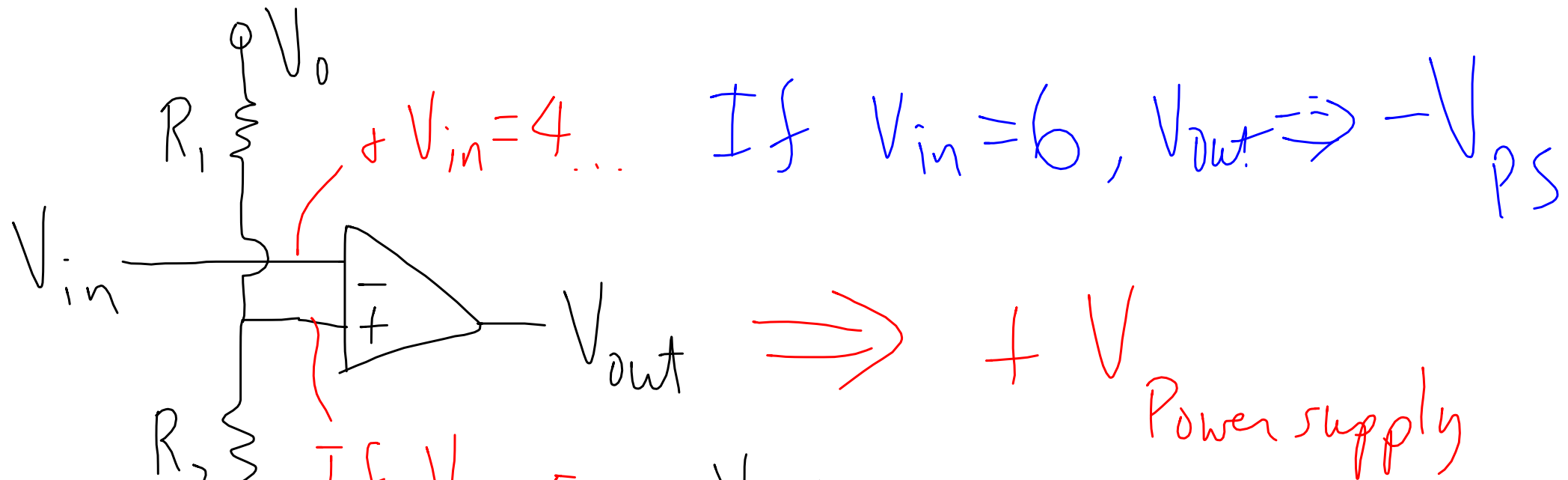

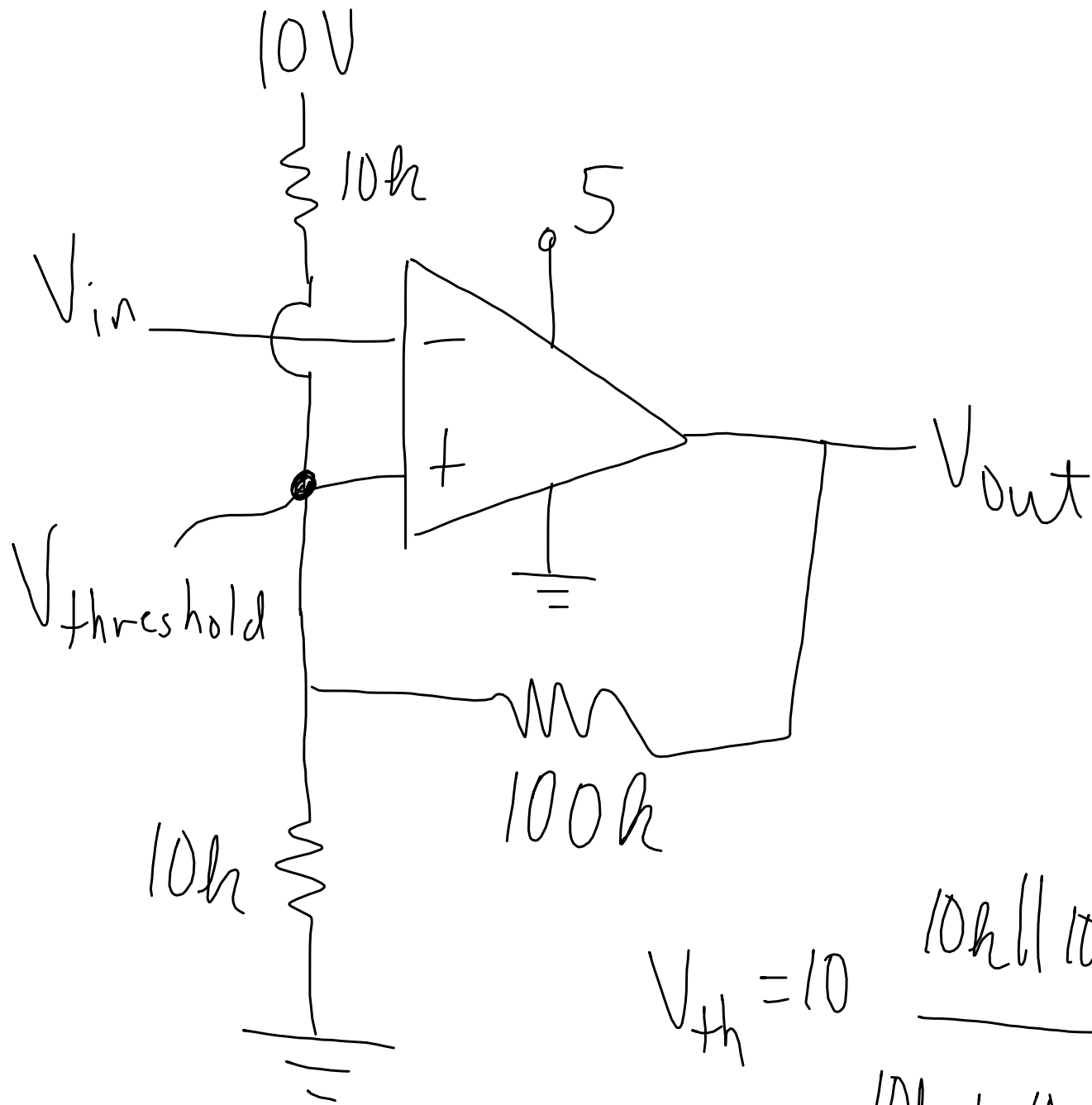



Assume V_{out} is 0.

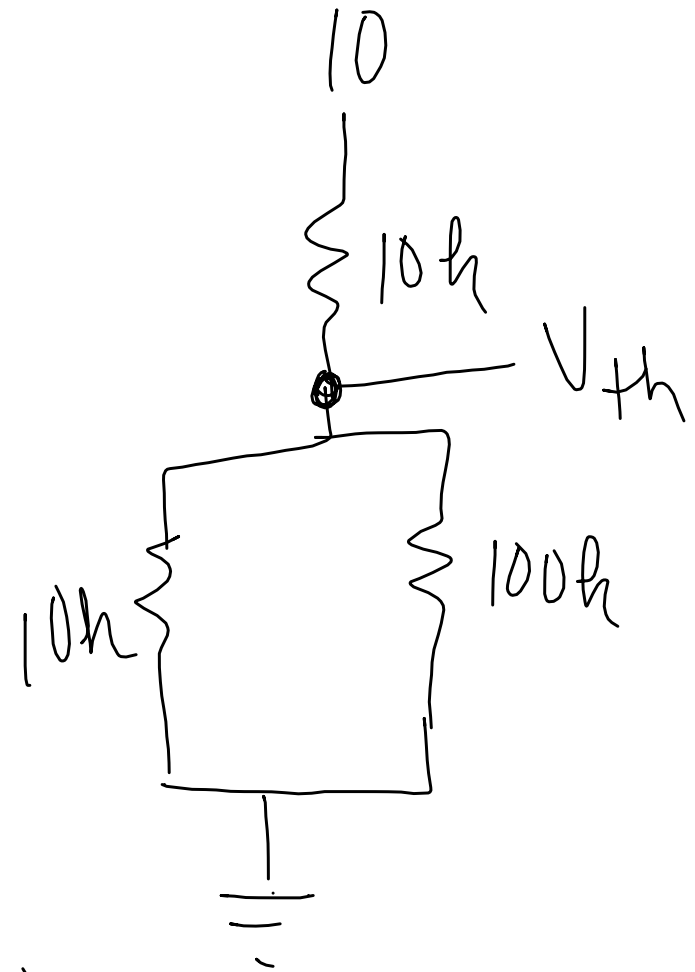


$$V_{th} = 10 \frac{10k \parallel 100k}{10k + 10k \parallel 100k}$$

$$\frac{(10k)(100k)}{110k} = 9.09k$$

$$= 4.76V$$

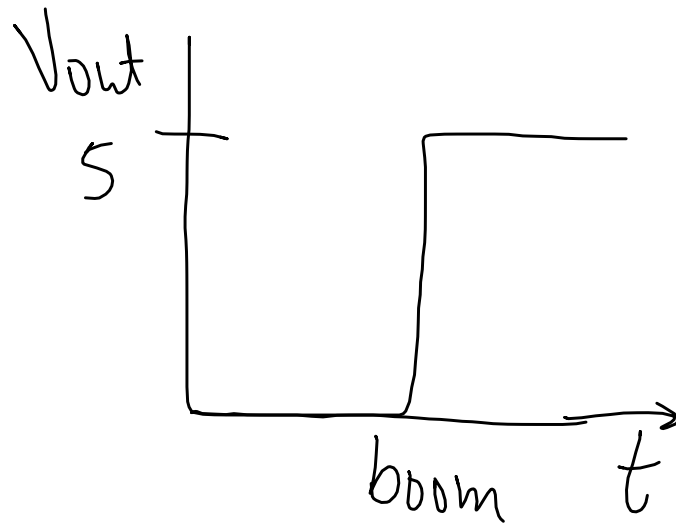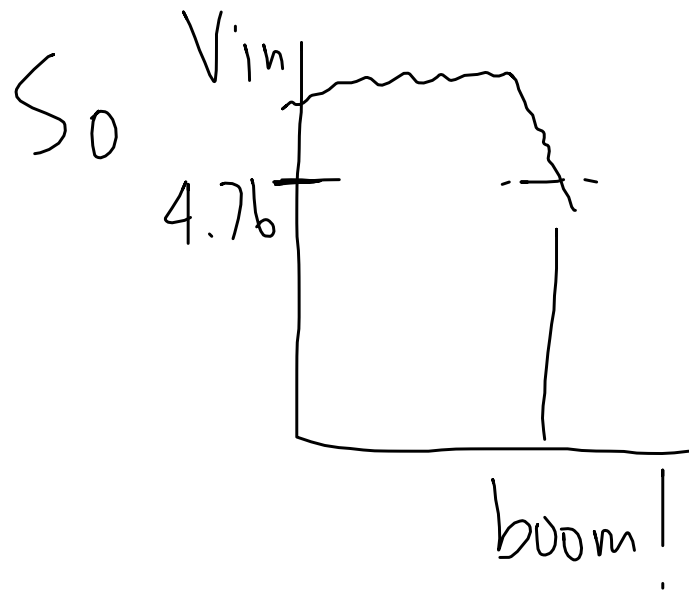

Now $V_{out} = 5V$. where is V_{th} ?

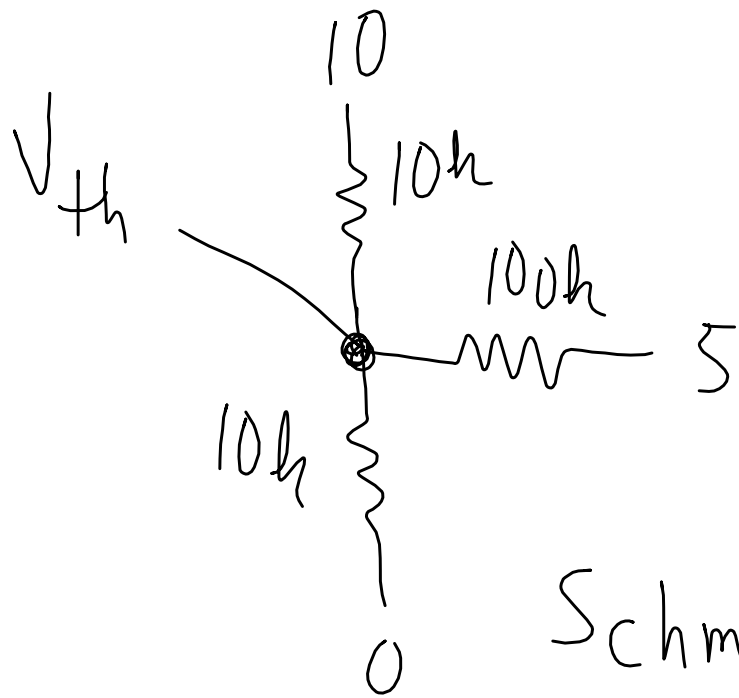


$$\frac{10 - V_{th}}{10k} + \frac{5 - V_{th}}{100k} + \frac{0 - V_{th}}{10k} = 0$$

$$10(10 - V_{th}) + 5 - V_{th} = 10V_{th}$$

$$105 = 21V_{th} \quad V_{th} = 5V$$

Schmitt
trigger

Looking ahead ...

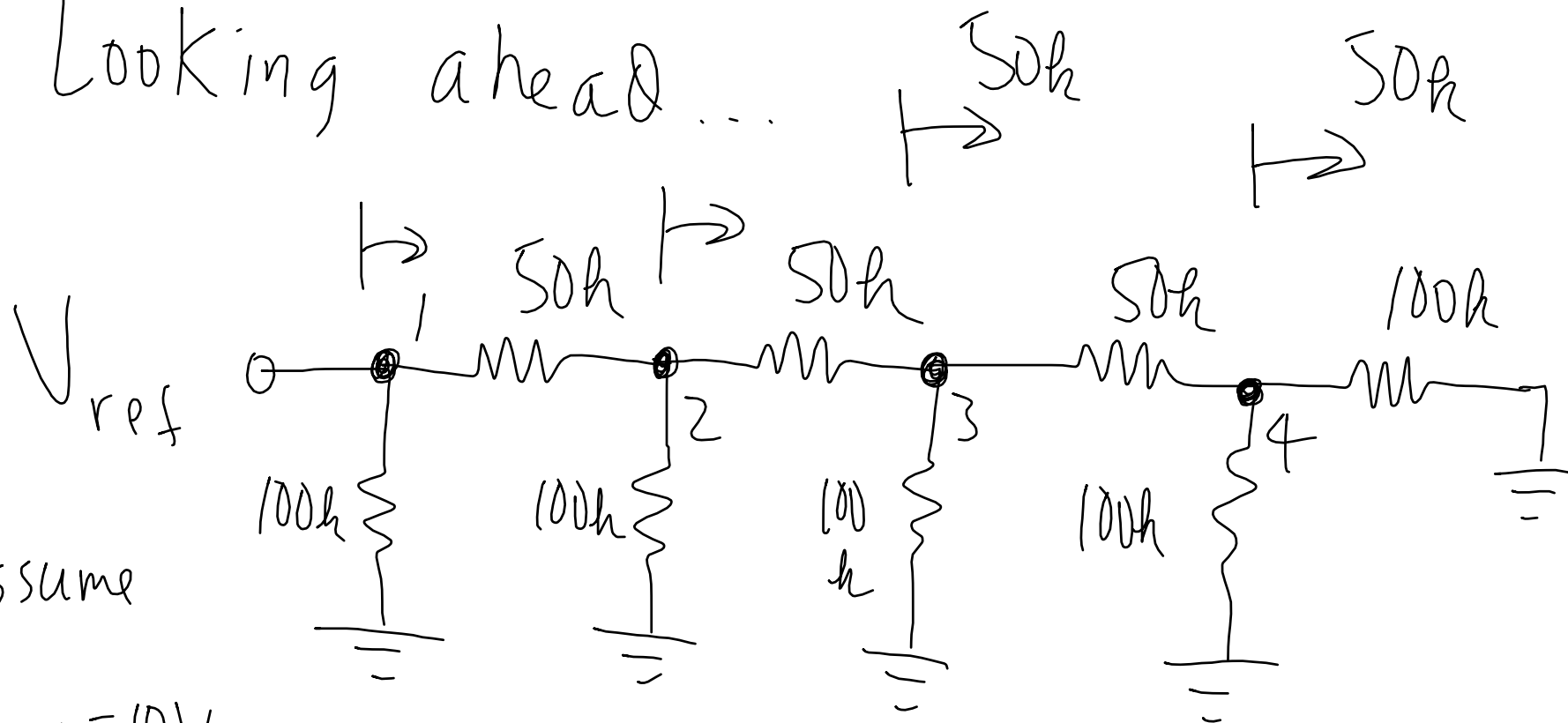

Assume

$$V_{ref} = 10V$$

$$V_1 = 10$$

$$V_2 = 5V$$

$$V_3 = 2.5V$$

$$V_4 = 1.25V$$